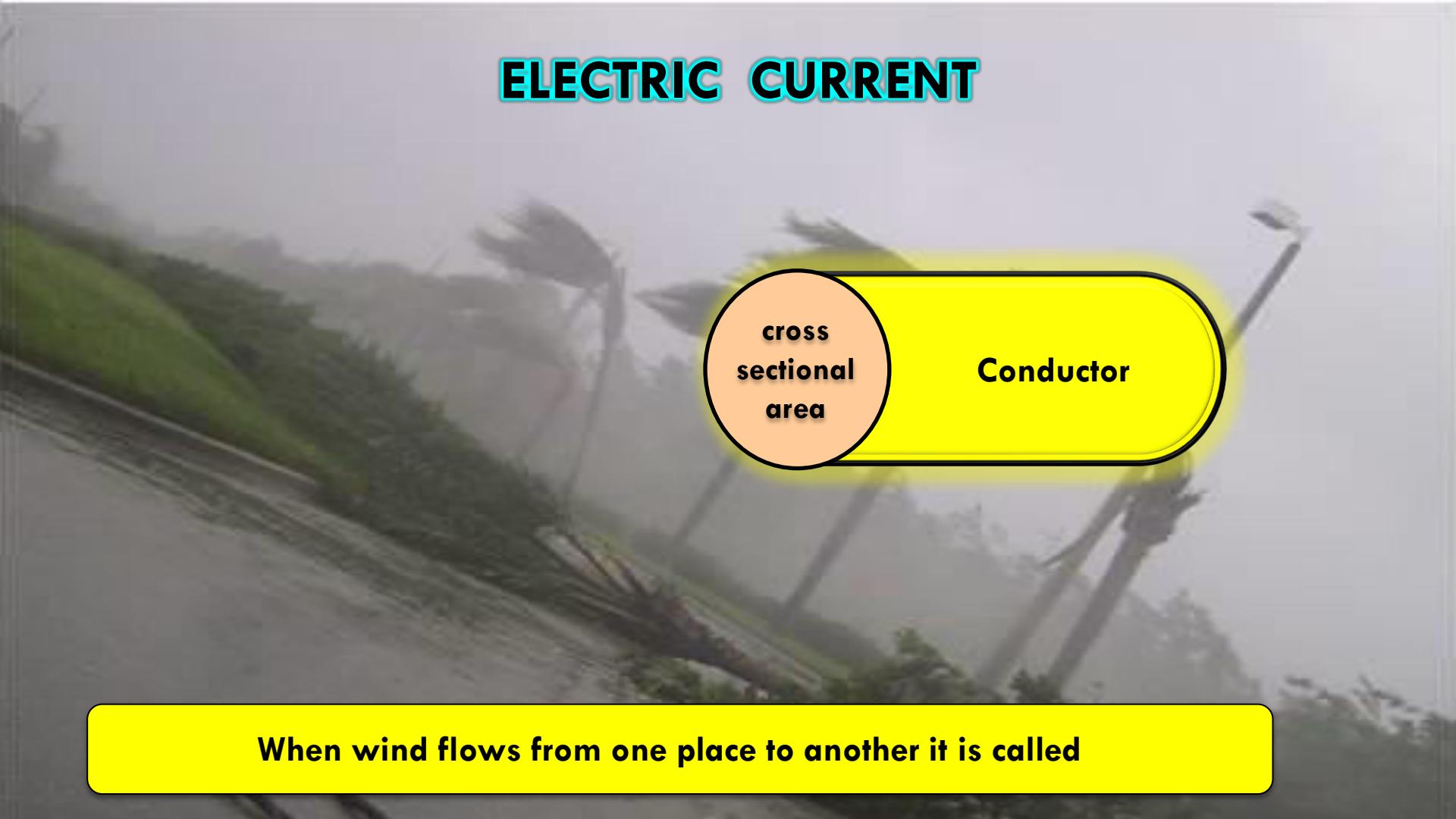


LECTURE 1

ELECTRIC CURRENT





A blurred background image of a road with palm trees and a yellow sign that is mostly illegible due to motion blur.

cross
sectional
area


Conductor

When wind flows from one place to another it is called

What makes the charge flow?

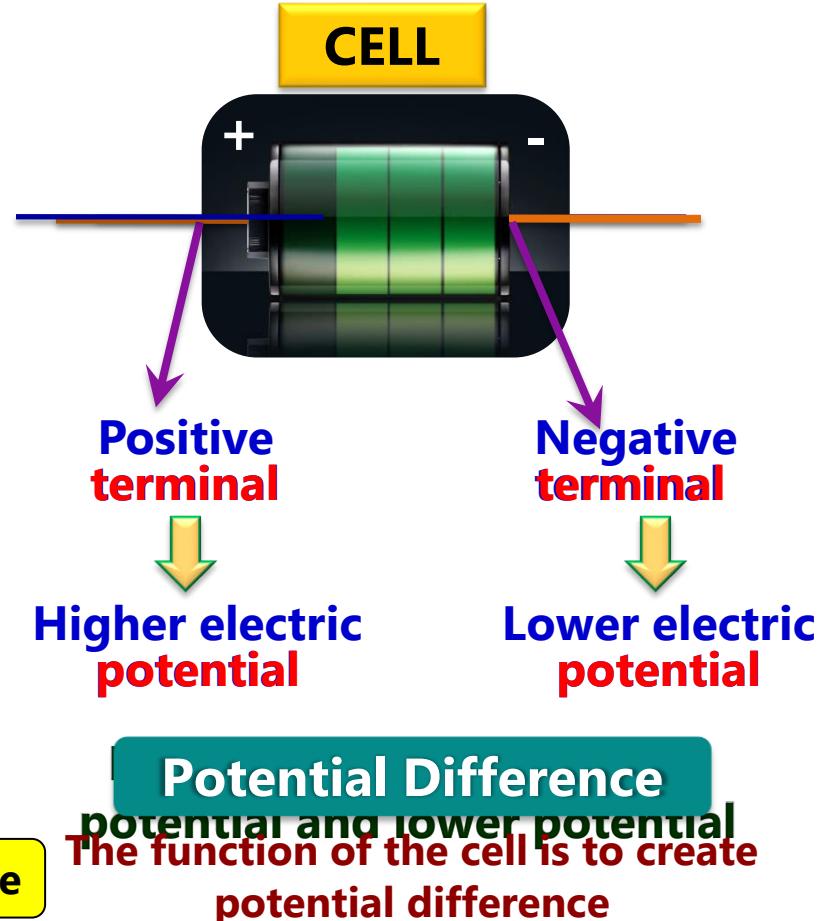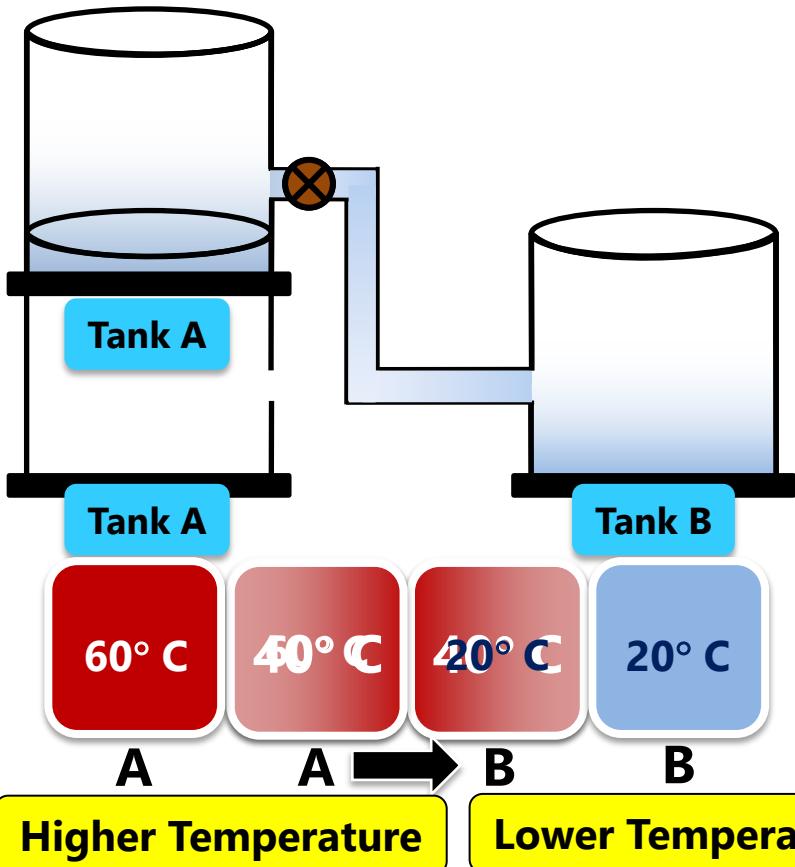

Now what is a free electron ?

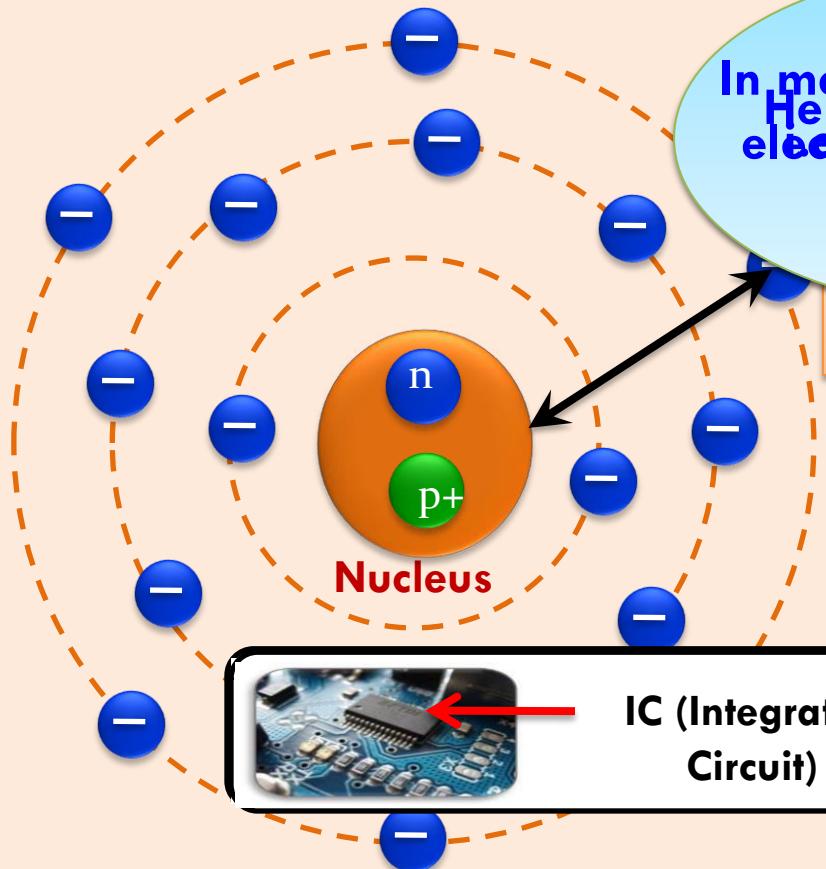

In metals the number of electrons is more.
Hence, electrons are lightly bound.

Depending on the number of free electrons, substances are classified into :

CONDUCTORS

Have large number of free electrons, which are charge carriers.

Have less or practically no free electrons



IC (Integrated Circuit)

They do not have free electrons at room temperature, but can develop under specific condition

A substance which does not allow charges to pass through it, easily is called as

- (a) metal
- (c) **insulator**

Insulators do not have free electrons

Negative term is

- (a) higher electric potential
- (c) pole

As they have concentration of negative charge

Conductor
Semiconductor

Substances which do not allow charges to pass through it but can develop under specific condition are called

- (a) metals
- (c) **semi conductors**

Free electrons are generated on imparting heat

- (a) **metals**
- (c) **conductors**


The function of the cell is _____

- (a) To create difference
- (c) **To create potential difference**


Cell creates potential difference

- (d) To develop free electrons

Flow of current in a Wire

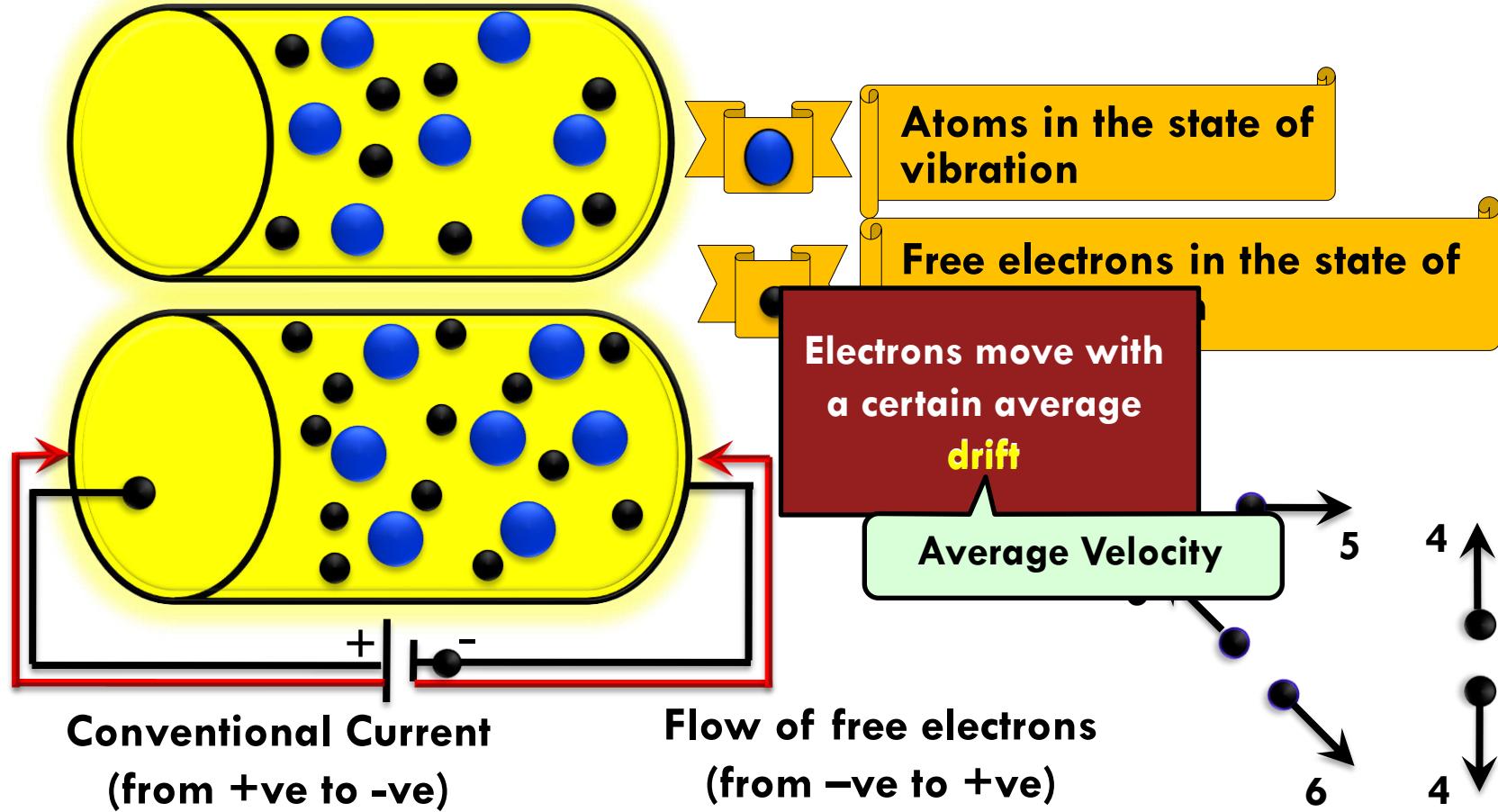


POTENTIAL DIFFERENCE

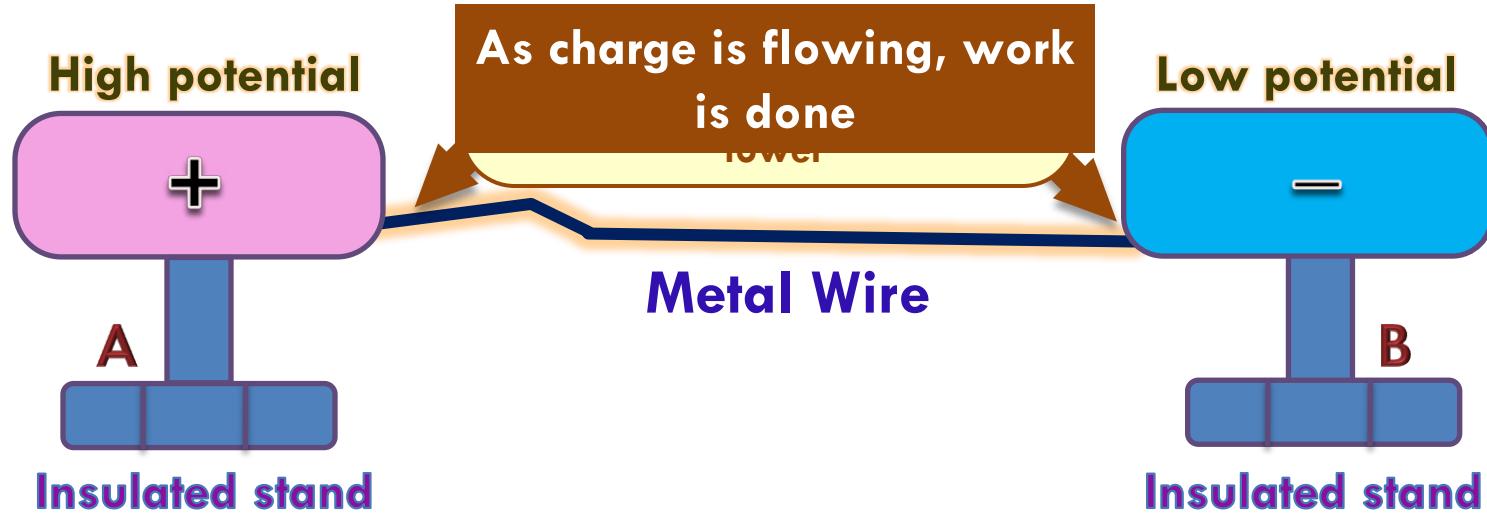

Potential Difference

The electric potential difference between two points in an electric Circuit is defined as the amount of the work done in moving a unit positive charge from one point to another point.

How does lightning occur

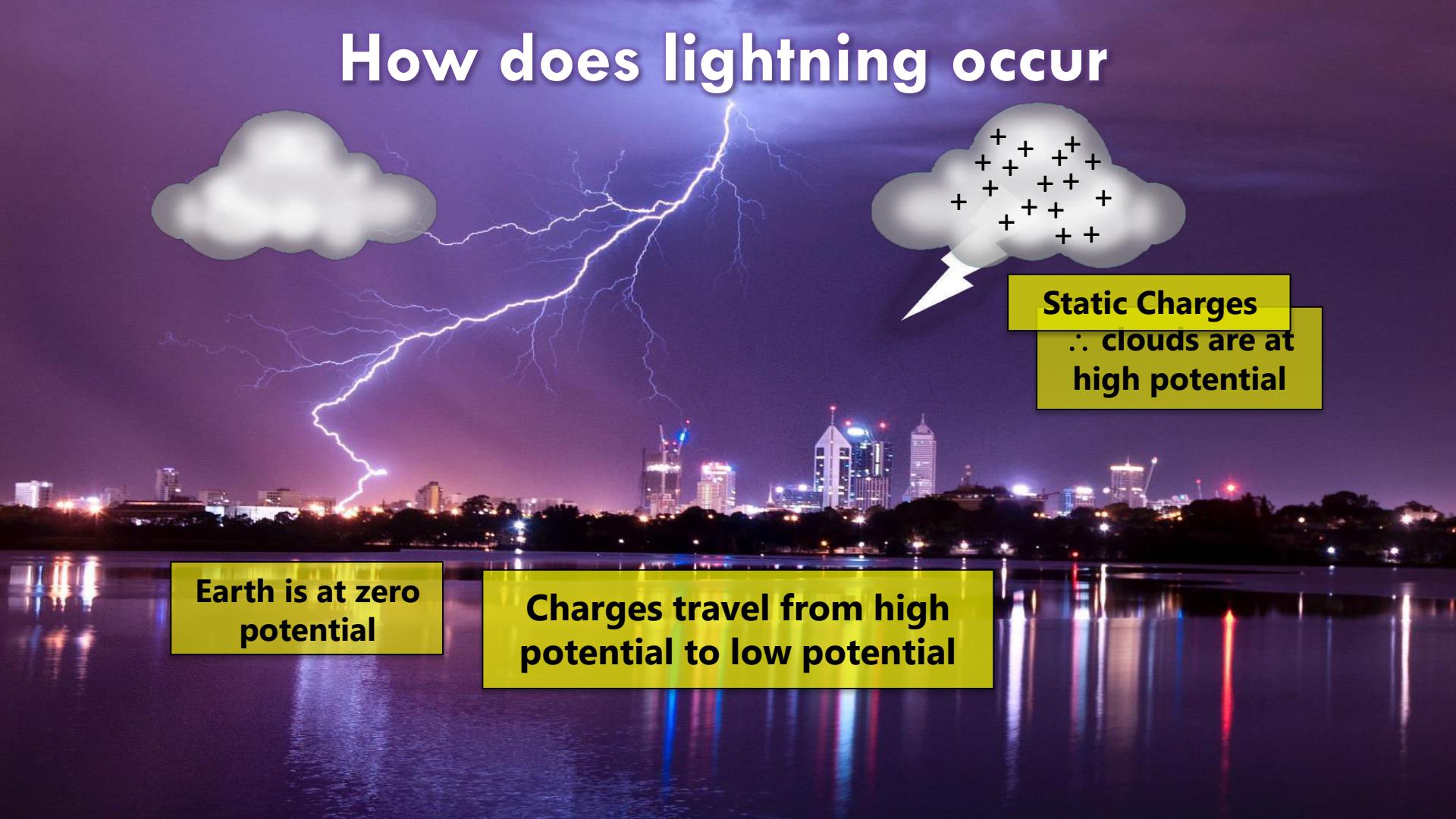



The electrons flow from negative terminal to positive terminal of the cell but the of current is from positive terminal to negative terminal of the cell.

- (a) conventional direction
- (c) real current

The function of the cell

- (a) potential difference
- (b) random motion of electrons
- (d) none of these

Conventional direction of current is opposite to the direction of flow of electrons

As cell c higher p and l potential

The potential of earth is

- (a) positive potential
- (b) zero potential
- (c) high potential
- (d) changes as per condition

As earth is a infinite body

Thank You

LECTURE 2

Physical Quantities



that can be
measured is a
PHYSICAL QUANTITY.



LOVE IS NOT A
**PHYSICAL
QUANTITY**

UNITS

Units are a system of measurement.



M.K.S. System

meter–kilogram–second



C.G.S. System

centimeter–gram–second



S.I. System

System International units

OR

Standard International units

coulomb (C) : S.I. unit of ELECTRIC CHARGE (Q)

- Two like point charges
- Equal magnitudes
- Placed in a vacuum
- Distance of one meter from each other
- Repel each other
- $9 \times 10^9 \text{ N} \cdot \text{m}^2 \cdot \text{C}^{-2}$
- Each charge is called



Sir COULOMB

The charge of an electron is $1.6 \times 10^{-19} \text{ C}$

The magnitude of charge on a particle is given by formula

$$Q = ne$$

Electrons measured by coulomb

∴ $n = \frac{Q}{1.6 \times 10^{-19}}$

∴ $n = 0.625 \times 10^{19}$

∴ $n = 6.25 \times 10^{18}$

Vacuum

volt (V) : S.I. unit of potential difference (V)




Scientist who discovered voltaic cell



or measuring potential difference

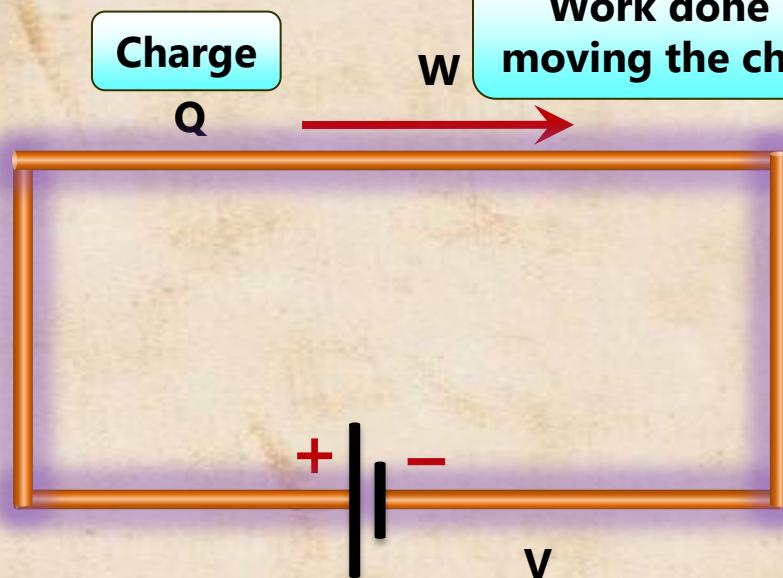volt (V) : S.I. unit of potential difference (V)



Work done in
moving the charge

Charge

Q

W

$$V = \frac{W}{Q}$$

$$1 \text{ volt} = \frac{1 \text{ joule}}{1 \text{ coulomb}}$$


$$1 \text{ V} = 1 \text{ J C}^{-1}$$

1 volt is the potential difference between two points in a current carrying conductor when 1 joule of work is done to move a charge of 1 coulomb from one point to another.

$$1 \text{ mV} = \frac{1}{1000 \text{ V}} = \frac{1}{10^3 \text{ V}} = 10^{-3} \text{ V}$$

$$\begin{aligned}1 \text{ kV} &= 10^3 \text{ V} \\1 \text{ MV} &= 10^6 \text{ V}\end{aligned}$$

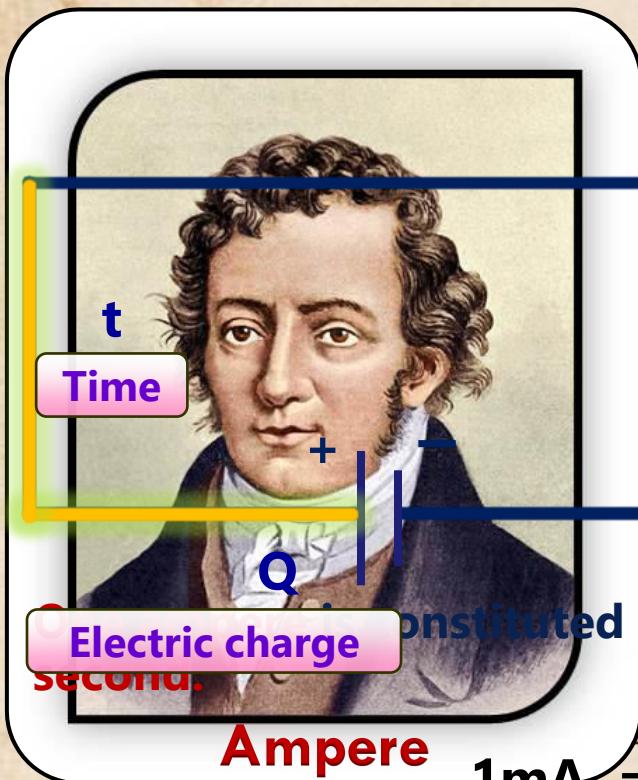ampere (A) : S.I. unit of ELECTRIC current (I)




Sir Andre Marie Ampere

$$I = \frac{Q}{t}$$

Electric Current = $\frac{\text{Electric Charge}}{\text{Time}}$

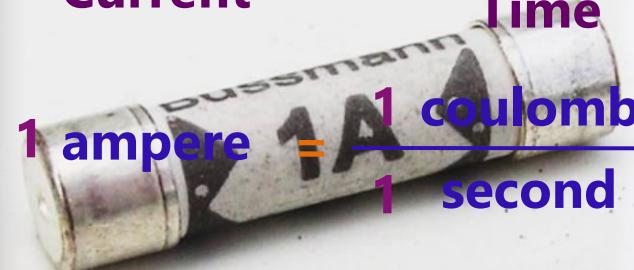1 ampere = $\frac{1 \text{ coulomb}}{1 \text{ second}}$



constituted by the flow of **one coulomb** of charge in **one second.**

unit for measuring electric current

$$1 \text{ mA} = \frac{1}{1000 \text{ A}} = \frac{1}{10^3 \text{ A}} = 10^{-3} \text{ A}$$

Match the following :

I

(i) Electric current (I)

(ii) Electric charge (Q)

(iii) Potential difference (V)

Answers

ampere

coulomb

volt

II



(a) joule (J)



(b) ampere (A)



(c) coulomb (C)



(d) volt (V)



Type - A

$$Q = It$$

$$W = VQ$$

$$Q = ne$$

Q.1. A current of 0.5 A is drawn by a filament of an electric bulb for 10 minutes. Find the amount of electric charge that flows through the circuit.

Given : Current (I) = 0.5 A

$$\begin{aligned}\text{Time (t)} &= 10 \text{ min} \\ &= 10 \times 60 \text{ sec.} \\ &= 600 \text{ sec.}\end{aligned}$$

To find : Charge (Q) = ?

Formula : Q = It

Solution : Q = It

$$\therefore Q = 0.5 \times 600$$

$$\therefore Q = 300 \text{ C}$$

The charge flowing through circuit is
300 C

Q.2. How much work is done in moving a charge of magnitude 2 C from a point at 118 volts to a point at 128 volts ?

Given : Charge (Q) = 2 C

Potential difference (V) = 128 V - 118 V = 10 V

To find : Work (W) = ?

Formula : $W = VQ$

Solution : $W = VQ$

$$\therefore W = 10 \times 2$$

$$\therefore W = 20 \text{ J}$$

The work done is 20 J

Q.3. Calculate the number of electrons constituting one coulomb of charge. OR

Show that 1 ampere is equivalent to flow of 6.25×10^{18} elementary charges

Given : Charge on an electron (e) = $1.6 \times 10^{-19} \text{ C}$

$$\text{Charge}(Q) = 1\text{C}$$

To find : No of electrons (n) = ?

Formula : $Q = ne$

Solution : $Q = ne$

$$\therefore n = \frac{1}{1.6 \times 10^{-19}}$$

$$\therefore n = 6.25 \times 10^{18}$$

Number of electrons constituting one coulomb of charge is 6.25×10^{18}

Q.4. How much work is done in moving a charge of magnitude 2 C across two point having a potential difference of 12 V ?

Given :

$$\text{Charge (Q)} = 2 \text{ C}$$

$$\text{Potential difference(V)} = 12 \text{ V}$$

To find : Work (W) = ?

Formula : $W = VQ$

Solution : $\therefore W = 12 \times 2$

$$\therefore W = 24 \text{ J}$$

The work done is 24 J

Q.5. How much energy is given to each coulomb of charge passing through 6 V battery ?

Given : Charge (Q) = 1C

Potential difference (V) = 6V

To find : Energy given by battery (W) = ?

Formula : $W = VQ$

Solution : $W = VQ$

$$\therefore W = 6 \times 1$$

$$\therefore W = 6 J$$

The energy given by battery is 6 J

Q.6. How many electrons are flowing per second past a point in a circuit in which there is a current of 5 amp ?

Given : Current (I) = 5 A

Time (t) = 1 sec

Charge on electron (e) = 1.6×10^{-19} C

To find : No of electrons (n) = ?

Formula : $Q = It$

$$Q = ne$$

Solution : $Q = It \dots \dots \dots \text{(i)}$

$$Q = ne \dots \dots \dots \text{(ii)}$$

From equation (i) and (ii)

$$It = ne$$

$$\therefore n = \frac{It}{e}$$

$$\therefore n = \frac{5 \times 1}{1.6 \times 10^{-19}}$$

$$\therefore n = 31.25 \times 10^{18}$$

Electrons flowing per second is
 31.25×10^{18}

Q.7. An electric heater is connected to the 230 V mains supply. A current of 8 A flows through the heater.

- (a) How much charge flows around the circuit in each second ?
- (b) How much energy is transferred to the heater in each second ?

Given : Potential

$$\text{difference (V)} = 230 \text{ V}$$

$$\text{Current (I)} = 8 \text{ A}$$

$$\text{Time (t)} = 1 \text{ sec}$$

To find : Charge (Q) = ?

$$\text{Energy (W)} = ?$$

Formula : $Q = It$

$$W = VQ$$

Solution : (a) $Q = It$

$$\therefore Q = 8 \times 1$$

$$\therefore Q = 8 \text{ C}$$

(b) $W = VQ$

$$\therefore W = 230 \times 8$$

$$\therefore W = 1840 \text{ J}$$

- (a) Charge flowing around the circuit is 8 C.
- (b) Energy transferred to the heater is 1840 J.

Thank You

LECTURE 3



OHM'S LAW


Ohms law states that, the current (I) flowing through a metallic conductor is directly proportional to the potential difference (V), across its ends provided its temperature remains the same.

**Length,
Area of cross section,
Temperature and
Material remain constant.**

V α I

$$\frac{V}{I} = \text{Constant}$$

= R (Resistance)

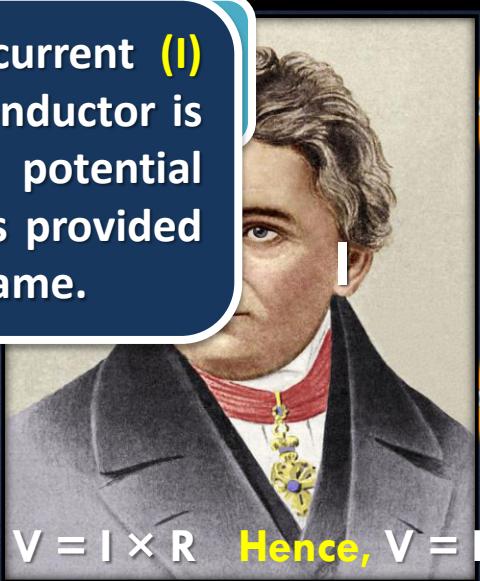


This is known as Ohm's law.




RESISTANCE

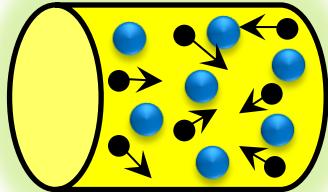The S.I. unit of RESISTANCE (R) is ohm (Ω)



$$R = \frac{V}{I}$$
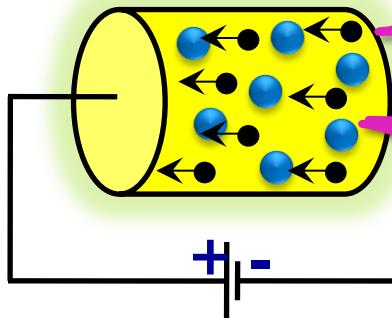
$$1 \text{ ohm} = \frac{1 \text{ volt}}{1 \text{ ampere}}$$



Current is more

The property of the conductor due to conductor which it opposes flow of current is

When atoms are less, more,
Resistance is less



FACTORS AFFECTING RESISTANCE




If the ride is thicker,
Hence R_a is more.
As R_a is more, flow
resistance becomes less.

Practical understanding of resistivity

1. Resistivity is a specific property of a material.

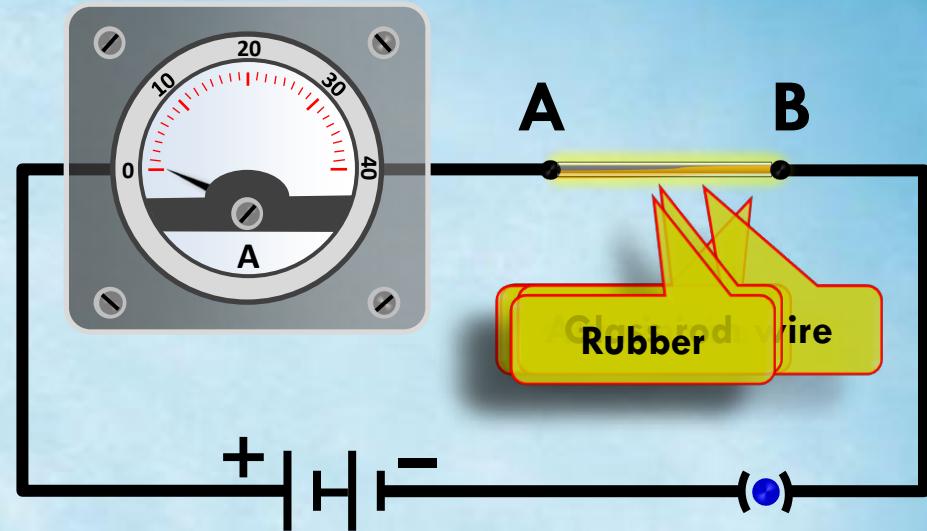2. Different materials have different resistivity



Electric Circuit

Q.1. On what factors does the resistance of a conductor depend?

Ans. : The resistance of a conductor depends on its

- i. Length
- ii. Area of cross – section (thickness)
- iii. Material
- iv. Temperature

Q.2. How does the resistance of a wire change when:

- (a) Its length is tripled?
- (b) Its diameter is tripled?
- (c) Its material is changed to one whose resistivity is three times?

Ans. : $R = \rho \frac{l}{A}$

(a) $R \propto l$

\therefore If l is tripled, resistance is also tripled.

(b) $R \propto \frac{1}{A}$ or

$$R \propto \frac{1}{d^2} \left(\because A = \pi r^2 = \frac{\pi d^2}{4} \right)$$

\therefore If the diameter is tripled
Resistance becomes $1/9$ times

(c) $R \propto \rho$

\therefore If resistivity is tripled,
resistance is also tripled

Q.3. Will current flow more easily through a thick wire or a thin wire of the same material, when connected to the same source? Why?


Ans. : (i) When connected to a same source, current will flow more easily through the thick wire than the thin wire.
(ii) Resistance $R \propto \frac{1}{A}$

Thank You

LECTURE 4

Circuit of television

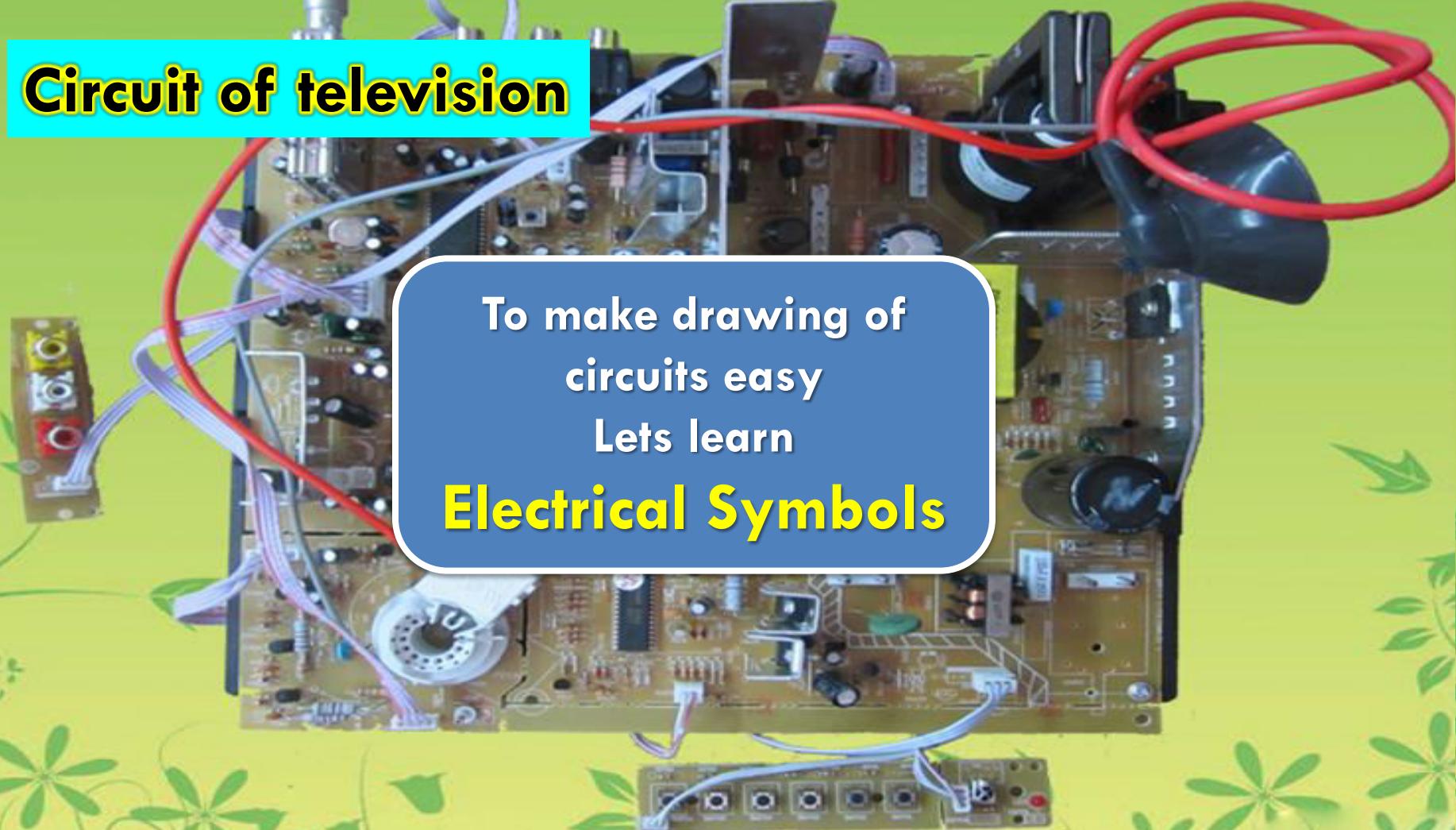To make drawing of
circuits easy
Lets learn
Electrical Symbols





ELECTRICAL SYMBOLS



Cell



Battery



Resistance



Variable
On
Resistance

KEYS / SWITCHES

Plug key



Closed (On)



Open (Off)



Measuring Instruments



Variable known Resistance



Ammeter



Voltmeter




Galvanometer






A wire joint

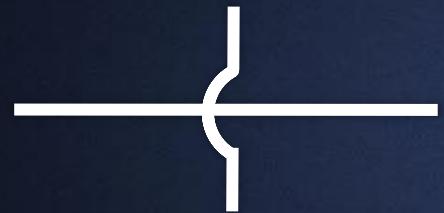

Wire crossing



Electric bulb

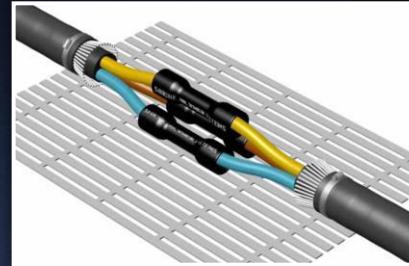



Draw the symbols of components required to make the circuit

Cell

Resistance

Battery

Ammeter

IT'S TEST TIME



Variable Resistance
(Unknown)



Variable Resistance
(known)



Voltmeter



Galvanometer



Plug key(on)



Tap key (on)



A wire joint



Electric bulb

Plug key(off)

Tap key (off)


Wire crossing



SOME IMPORTANT POINTS TO REMEMBER



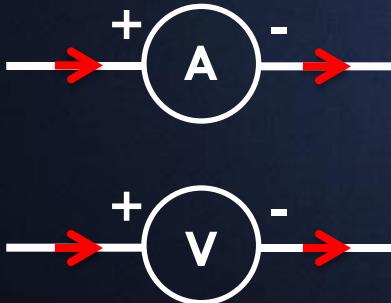
While connecting cells to each other always connect unlike terminals.



For devices like ammeter or voltmeter, the side from which current enters is positive (+) and the side from which current exits is negative (-).



SOME IMPORTANT POINTS TO REMEMBER

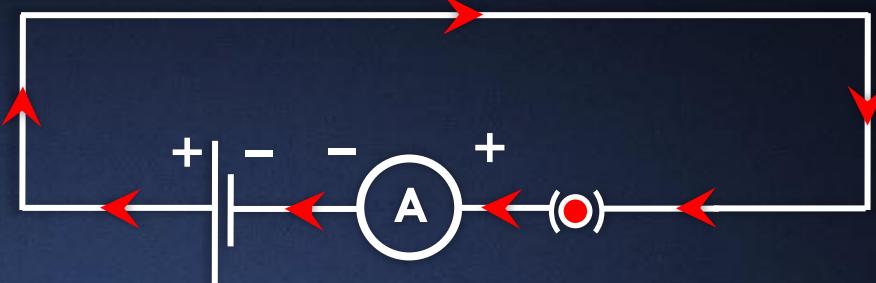


So the current in the circuit is not divided as the resistance of the ammeter is negligible for it to measure.

As the current in the circuit is not divided I.



current in the circuit is divided
Ammeter

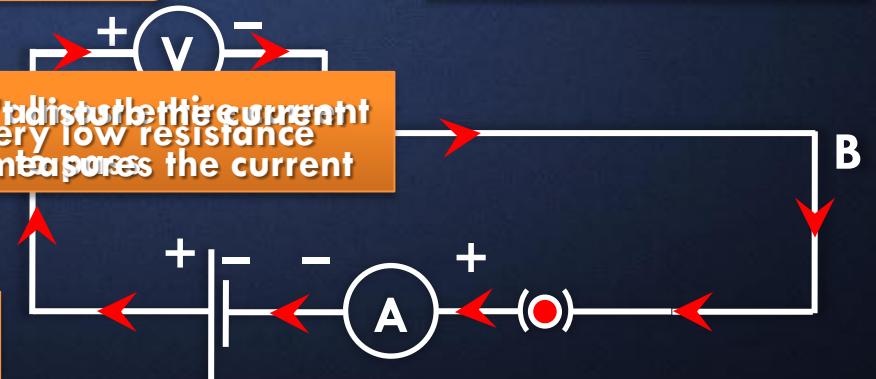So it doesn't disturb the current
It has very low resistance
as well as measures the current



Voltmeter is connected in parallel with the cell.

Q.1. How is a voltmeter connected in the circuit to measure the potential difference between two points?

Ans. : To measure the potential difference between two points, voltmeter must always be connected in parallel to the points.


Q.2. What happens if an ammeter is connected in parallel?

Ans. : If an ammeter is connected in parallel, the resultant resistance of the circuit decreases and more current passes through the ammeter. Hence, the ammeter is likely to be burnt.

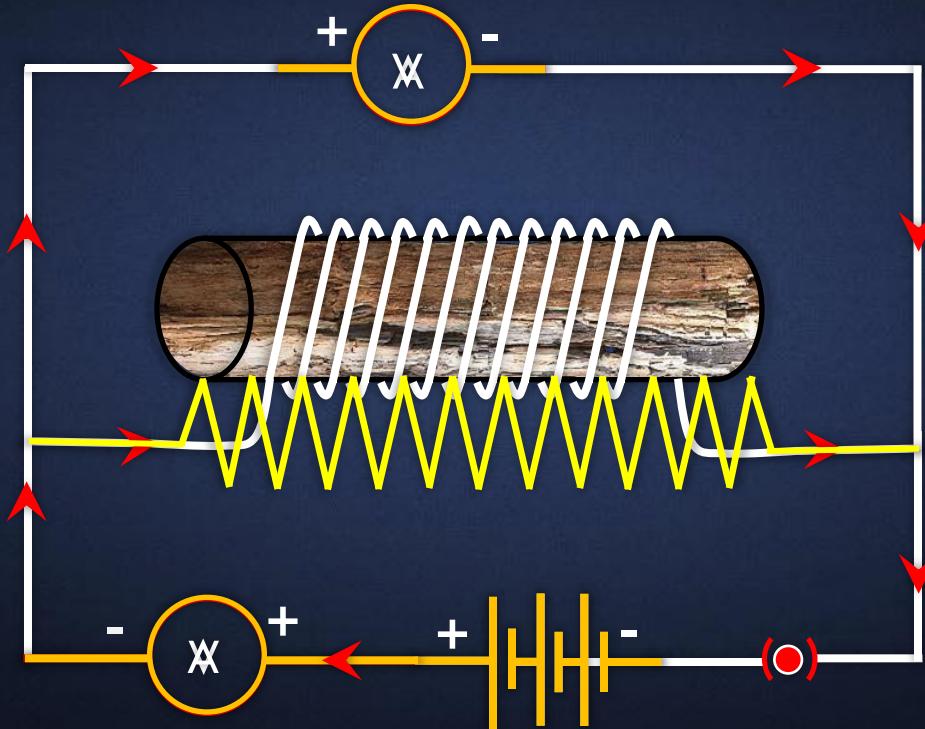Q.3. What happens if a voltmeter is connected in series?


Ans. : When the voltmeter is connected in series, the resistance of the circuit becomes high and there is considerable fall in current through the circuit. Thus, the voltmeter will not give the correct reading of the potential difference.

How many mistakes can you find in this diagram






Experimental verification of Ohm's law

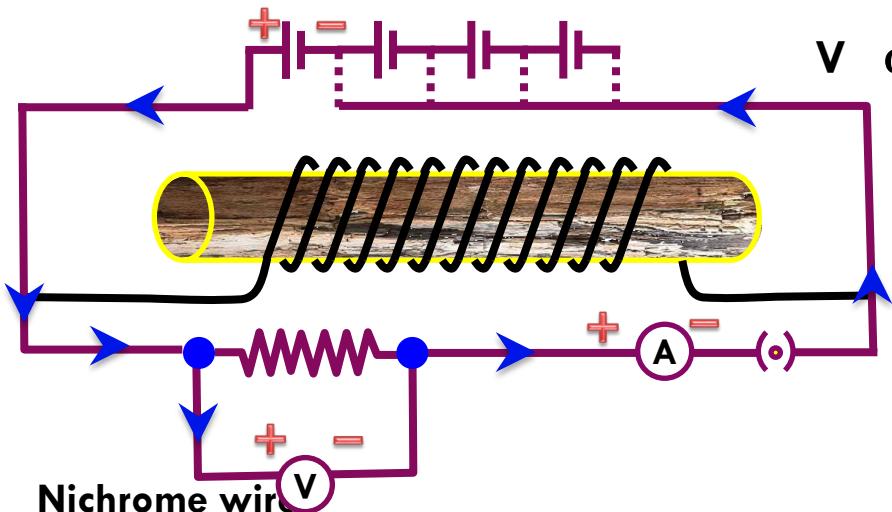

Nichrome wire


No of Cells	I (A)	P.D (V)	$\frac{V}{I} = R (\Omega)$
1	1	2	2
2	2	4	2
3	3	6	2

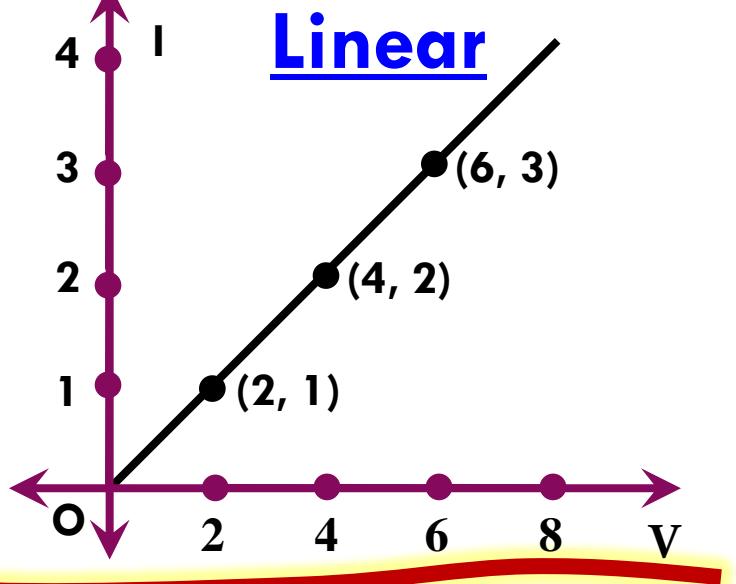$V \propto I$ and $\frac{V}{I} = R$ (Constant)



Thank You

LECTURE 5

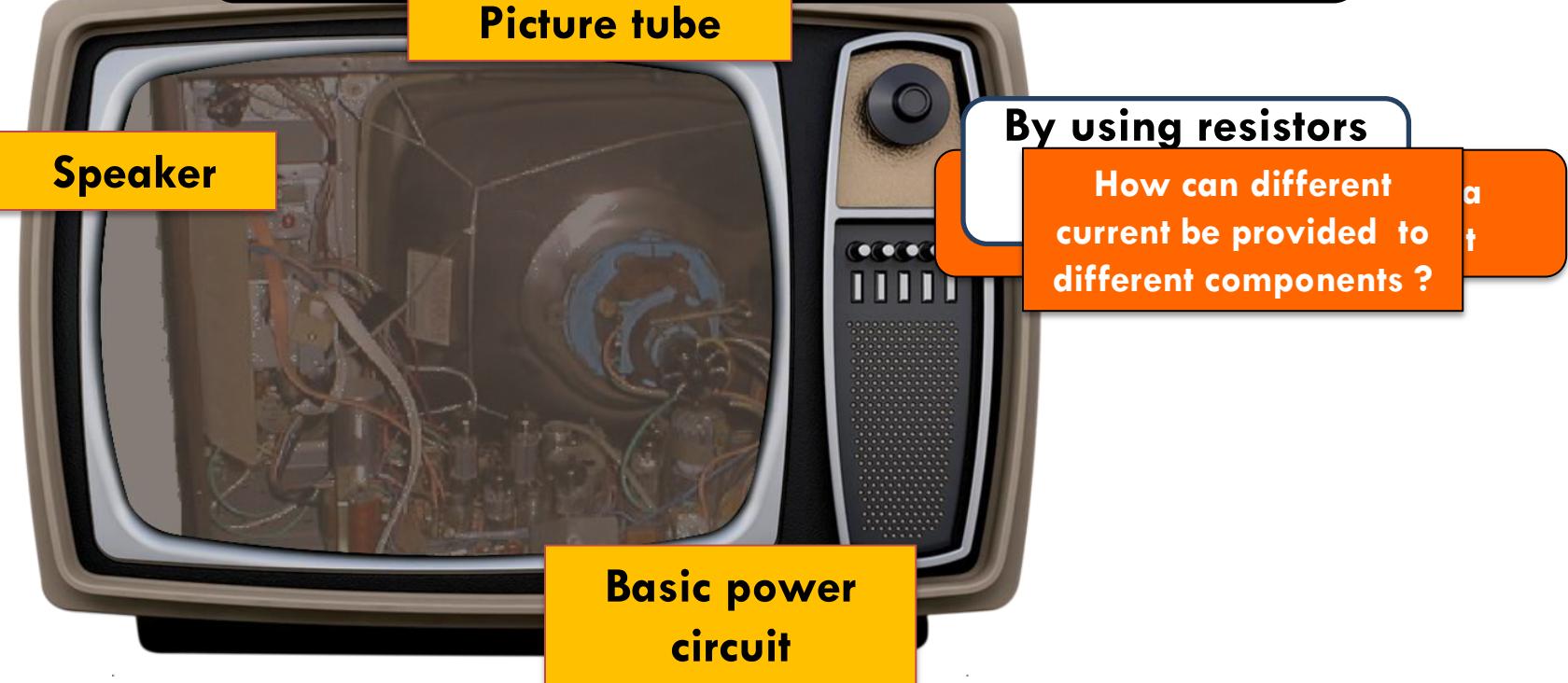

Old CRT television television which is a combination of many components.

Picture tube

Speaker


By using resistors

How can different current be provided to different components ?

Resistances can be connected in two ways

SERIES

One after the other

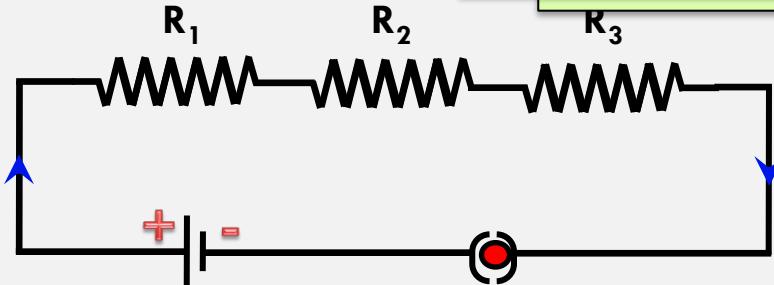


Current gets divided but potential difference remains the same

Potential drop difference

PARALLEL

between two common points

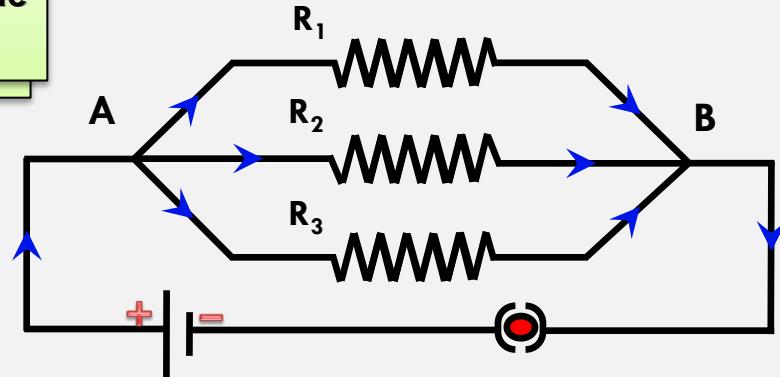

According to OHM'S LAW,

$$V = IR_s , V_1 = IR_1 , V_2 = IR_2 \text{ & } V_3 =$$

Substituting the values of V , V_1 , V_2 and V_3 in equation (i), we get

IR_s = IR₁ + IR₂ DERIVE A FORMULA FOR EFFECTIVE RESISTANCE

∴ ~~IR~~_s FOR THREE RESISTANCES CONNECTED IN SERIES AND PROVE THAT


$\therefore R_s = R_1 + R_2 + R_3$ Where R_s is the

“Effective Resistance in Series”.

For 'n' number of resistances, we have


$$R_s = R_1 + R_2 + R_3 + \dots + R_n$$

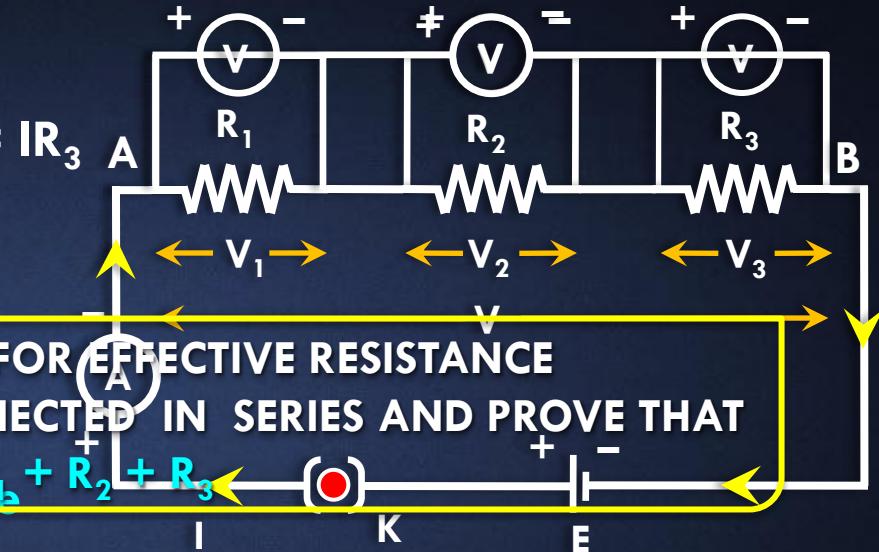Effective Resistance in series (R_s) is the sum of the individual resistances.





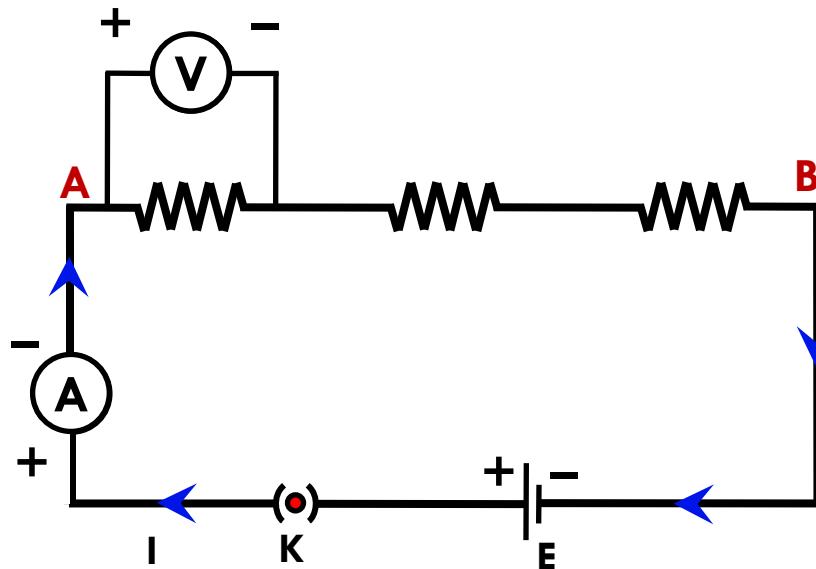Draw this diagram and make the required corrections





Write the derivation of resistance in series

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 + \mathbf{V}_3 \dots \dots \dots \text{(i)}$$

According to OHM'S LAW,

$$V = IR_s, V_1 = IR_1, V_2 = IR_2 \text{ & } V_3 = IR_3$$

00: 00

Substituting the values of V , V_1 , V_2

and V_3 in equation (i), we get

$$IR_s = IR_1 + IR_2 + IR_3$$

$$\therefore \text{IR}_s = I(R_1 + R_2 + R_3)$$

$\therefore R_s = R_1 + R_2 + R_3$ Where R_s is the

“Effective Resistance in Series”.

For 'n' number of resistances, we have

$$R_s = R_1 + R_2 + R_3 + \dots + R_n$$

Effective Resistance in series (R_s) is the sum of the individual resistances.

$$I = I_1 + I_2 + I_3 \quad \text{----- (i)}$$

According to OHM'S LAW,


$$V = IR, I = \frac{V}{R_p}, I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3}$$

Substituting the values of I , I_1 , I_2 and I_3 in equation (i), we get

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

DERIVE A FORMULA FOR EFFECTIVE RESISTANCE FOR THREE RESISTANCES CONNECTED IN PARALLEL AND PROVE THAT

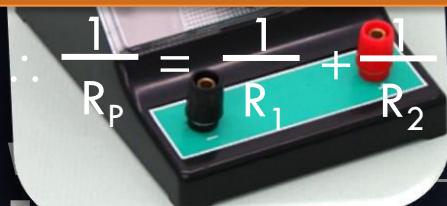
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



"Reciprocal of Effective Resistance in Parallel".

For n number of resistances, we have
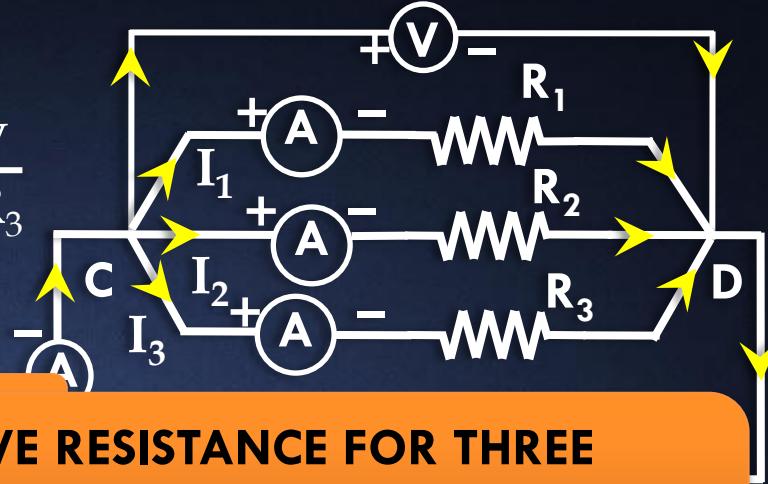
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$



The reciprocal or effective Resistance in Parallel (R_p) is the sum of the reciprocals of the individual resistances.



Write the derivation of resistance in parallel

$$I = I_1 + I_2 + I_3 \quad \dots \quad (i)$$

According to OHM'S LAW,

$$I = V/R_p, I_1 = V/R_1, I_2 = V/R_2 \quad \& \quad I_3 = V/R_3$$

Substituting the values of I , I_1 , I_2 and I_3 in equation (i), we get

$$V/R_p = V/R_1 + V/R_2 + V/R_3$$

$$\therefore \cancel{V}/R_p = \cancel{V}(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3})$$

$\therefore 1/R_p = 1/R_1 + 1/R_2 + 1/R_3$ Where R_p is the "Effective Resistance in Parallel".

For 'n' number of resistances, we have

$$1/R_p = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_n$$


The reciprocal of Effective Resistance in parallel (R_p) is the sum of reciprocal of individual resistances.

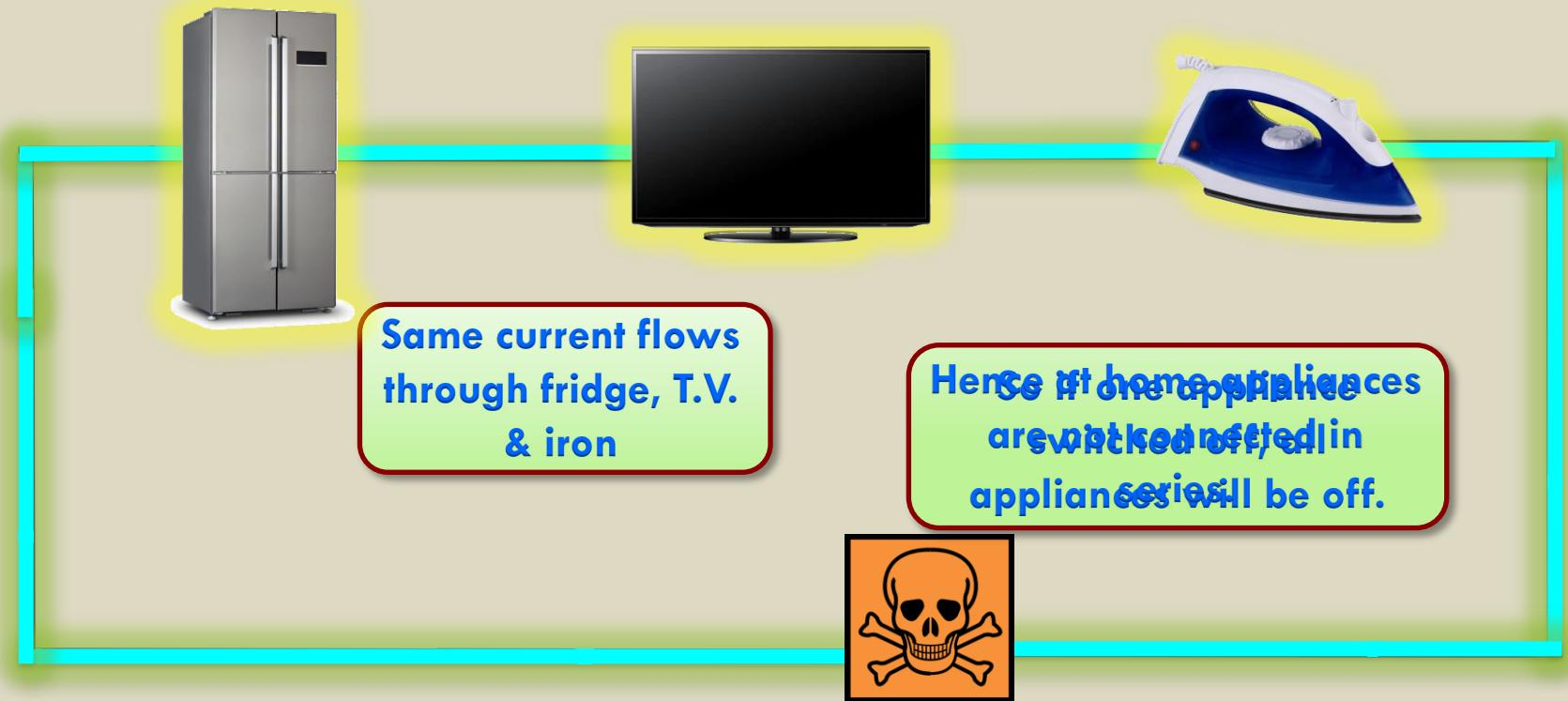00: 00


How are the appliances connected at home, series or parallel




What will happen, if appliances (resistors) are connected in series ?



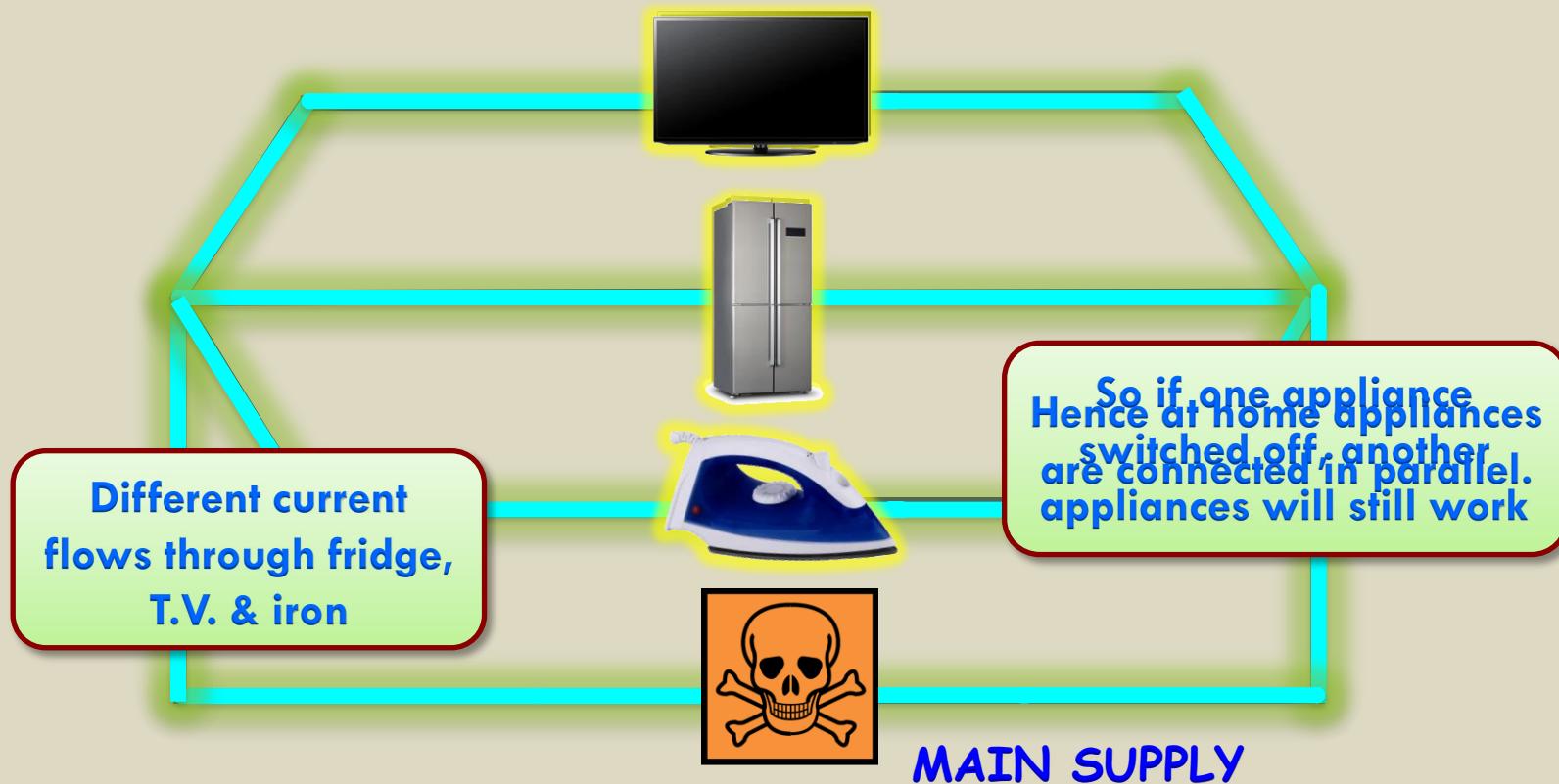What will happen, if appliances (resistors) are connected in parallel ?



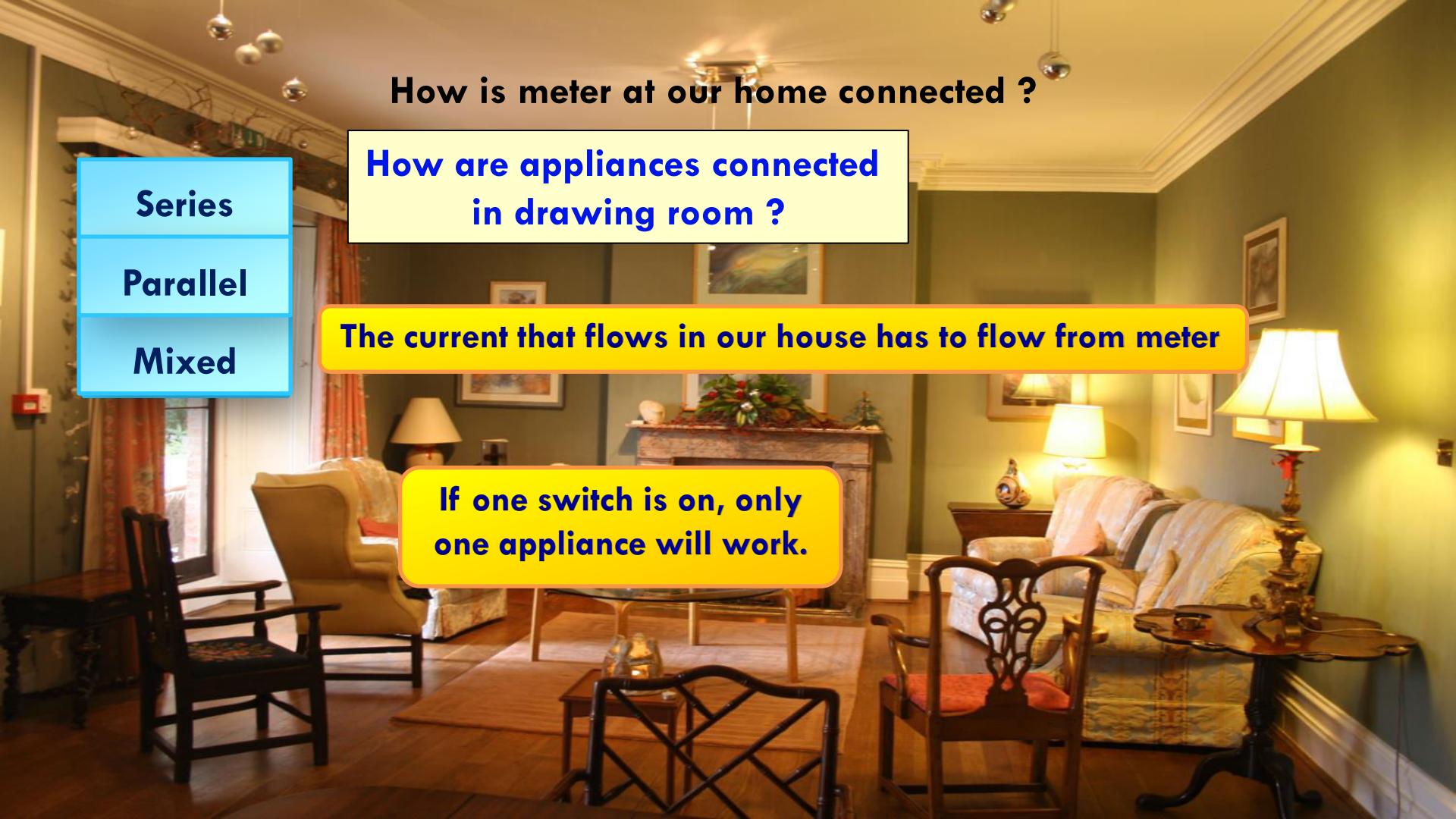

How is meter at our home connected ?

Series

Parallel

Mixed

**How are appliances connected
in drawing room ?**

The current that flows in our house has to flow from meter

If one switch is on, only
one appliance will work.

Q.1.What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?

- Ans. :**
- i. When a number of electrical devices are connected in parallel, each device gets the same potential as the supplied voltage. Due to this, other devices are not affected if one device fails. In series connection, if one device fails, the circuit breaks and others stop working.
 - ii. The parallel circuit divides the current through the electrical devices. Thus each device gets proper current depending on its resistance. Whereas, in series circuit, same current flows through all the devices, irrespective of their resistance.
 - iii. The total circuit resistance can be reduced by connecting the devices in parallel.

Thank You

LECTURE 6



TYPE - C

$$R_s = R_1 + R_2 + R_3$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Q.1. A battery of 9V is connected in series with resistance of 0.2Ω , 0.3Ω , 0.4Ω , 0.5Ω and 12Ω respectively. How much current would flow through the 12Ω resistor ?

Given : Total resistance, $R = 0.2 + 0.3 + 0.4 + 0.5 + 12 = 13.4\Omega$
 $V = 9V$

To find : Current (I) = ?

Formula : $V = IR$

Solution : $I = \frac{V}{R}$

$$= \frac{9}{13.4}$$

$$= 0.67 \text{ A}$$

Current through 12Ω resistor = 0.67A .

Q2. Judge the equivalent resistance when the following are connected in parallel :

(a) 1Ω and $10^6\Omega$

(b) 1Ω and $10^3\Omega$ and $10^6\Omega$

Ans. : (a) 1Ω and $10^6\Omega$ are connected in parallel.

$$\therefore \frac{1}{R} = \frac{1}{1} + \frac{1}{10^6} = \frac{10^6 + 1}{10^6}$$

\therefore Equivalent Resistance $\approx 1\Omega$
(but less than 1Ω)

$$\therefore R = \frac{10^6}{10^6 + 1} \approx \frac{10^6}{10^6}$$
$$\approx 1\Omega$$

(b) 1Ω , $10^3\Omega$ and $10^6\Omega$ are in parallel.

$$\therefore \frac{1}{R} = \frac{1}{1} + \frac{1}{10^3} + \frac{1}{10^6}$$

$$\therefore \frac{1}{R} = \frac{10^6 + 10^3 + 1}{10^6}$$

$$\therefore R = \frac{1000000}{1001001}$$

$$\therefore R = 0.999 \Omega$$

\therefore Equivalent Resistance = 0.999Ω

Q.3. An electric lamp of 100Ω , a toaster of resistance 50Ω , and a water filter of resistance 500Ω are connected in parallel to a $220V$ source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it?

Given : Resistance of lamps = $R_1 = 100\Omega$
Resistance of toaster = $R_2 = 50 \Omega$
Resistance of filter = $R_3 = 500 \Omega$
 $V = 220V$

To find : Resistance of iron, Current through iron

Formula : $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$, $V = IR$

Solution : Let R be the equivalent resistance,

$$\begin{aligned}\frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{100} + \frac{1}{50} + \frac{1}{500} \\ &= \frac{5 + 10 + 1}{500} = \frac{16}{500}\end{aligned}$$

$$\therefore R = \frac{500}{16}$$

According to Ohm's law, $V = IR$

$$\therefore I = \frac{V}{R} = \frac{220}{500} = \frac{220 \times 16}{500} = 7.04A$$

7.04 A current is drawn by all three appliances.

\therefore Current drawn by an electric iron connected to the same source of P.D. $220V = 7.04A$

\therefore It's Resistance,

$$R = \frac{V}{I} = \frac{220}{7.04} = 31.25\Omega$$

\therefore Current flowing through iron = $7.04A$
Resistance of iron = 31.25Ω

Q.4. How can three resistors of resistance 2Ω , 3Ω and 6Ω be connected to give a total resistance of (a) 4Ω , (b) 1Ω ?

Ans. : $R_1 = 2\Omega$, $R_2 = 3\Omega$, $R_3 = 6\Omega$

(a) To get $R_e = 4\Omega$, the circuit is as shown,

R_2 and R_3 are in parallel

$$\therefore \frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{3} + \frac{1}{6}$$


$$\frac{1}{R_p} = \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$\therefore R_p = 2\Omega$$

R_p and R_1 are in series

$$\begin{aligned}\therefore R_e &= R_p + R_1 \\ &= 2 + 2\end{aligned}$$

$$R_e = 4\Omega$$

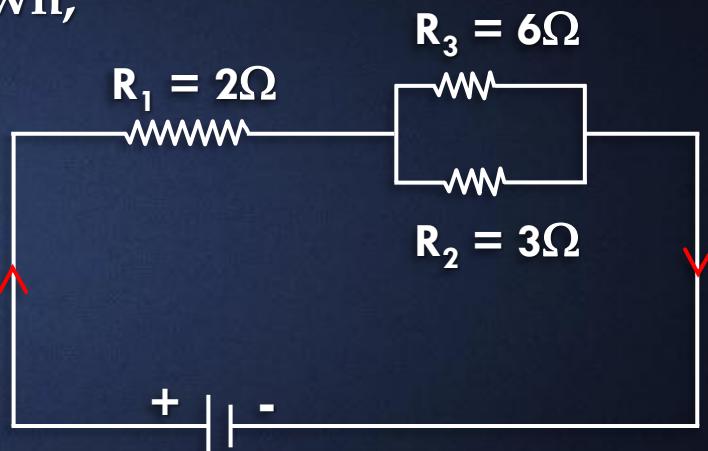


Q.4. How can three resistors of resistance 2Ω , 3Ω and 6Ω be connected to give a total resistance of (a) 4Ω , (b) 1Ω ?

Ans. : (b) To get $R_e = 1\Omega$, the circuit is as shown,

$$\begin{aligned}\frac{1}{R_e} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{2} + \frac{1}{3} + \frac{1}{6} \\ &= \frac{2+3+1}{6} \\ &= \frac{6}{6} = 1\Omega\end{aligned}$$

$$\therefore R_e = 1\Omega$$

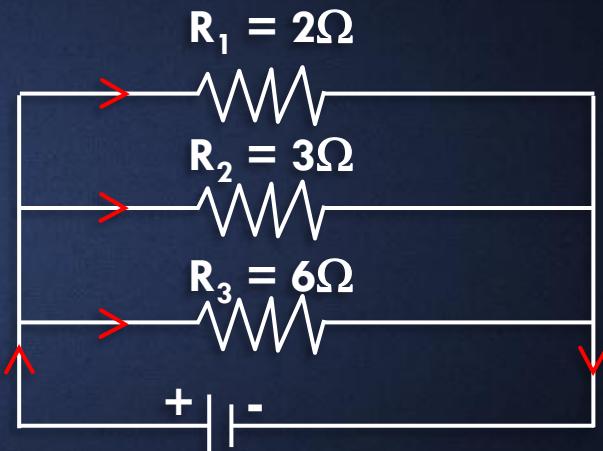

5

An electric lamp, whose resistance is $20\ \Omega$, and a conductor of $4\ \Omega$ resistance are connected to a 6 V battery. Calculate

- the total resistance of the circuit,
- the current through the circuit, and
- the potential difference across the electric conductor and lamp

Given :

$$\text{Resistance of electric lamp, } (R_1) = 20\ \Omega$$

$$\text{Resistance of conductor, } (R_2) = 4\ \Omega$$

$$\text{Potential difference (V)} = 6\text{ V}$$

To find : (a) total resistance (R) = ?


(b) Current (I) = ?

(c) potential difference across lamp (V_1) = ?

potential difference across conductor (V_2) = ?

Formulae : $R_s = R_1 + R_2$

$V = IR$

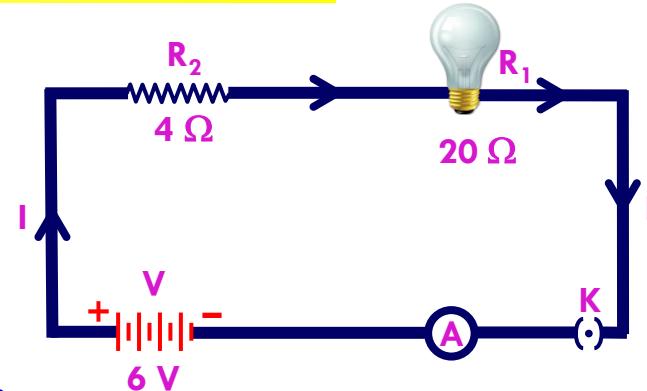

5

An electric lamp, whose resistance is $20\ \Omega$, and a conductor of $4\ \Omega$ resistance are connected to a 6 V battery. Calculate

- the total resistance of the circuit,
- the current through the circuit, and
- the potential difference across the electric conductor and lamp

Solution :

(a) Total resistance (R_s)

$$R_s = R_1 + R_2$$

$$\therefore R_s = 20 + 4$$

$$\therefore R_s = 24\ \Omega$$

(b) Total current (I)

$$I = \frac{V}{R_s}$$

$$\therefore I = \frac{6}{24}$$

$$\therefore I = 0.25\text{ A}$$

(c) (i) P.D. across the electric lamp

$$V_1 = I \times R_1$$

$$\therefore V_1 = 0.25 \times 20$$


$$\therefore V_1 = 5\text{ V}$$

(ii) P.D. across the electric conductor

$$V_2 = I \times R_2$$

$$\therefore V_2 = 0.25 \times 4$$

$$\therefore V_2 = 1\text{ V}$$

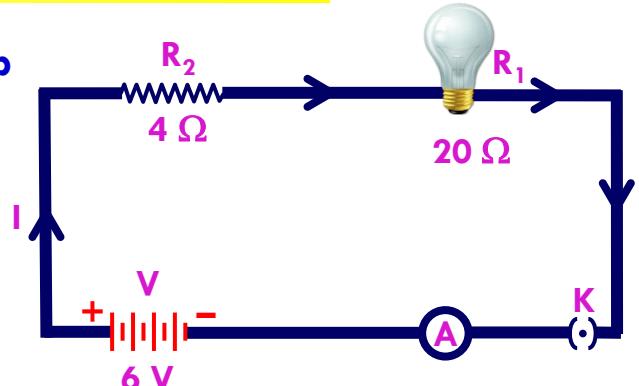


Ans :

Total resistance is $24\ \Omega$, Total current is 0.25 A , P.D across lamp is 5 V , P.D across conductor is 1 V .

6

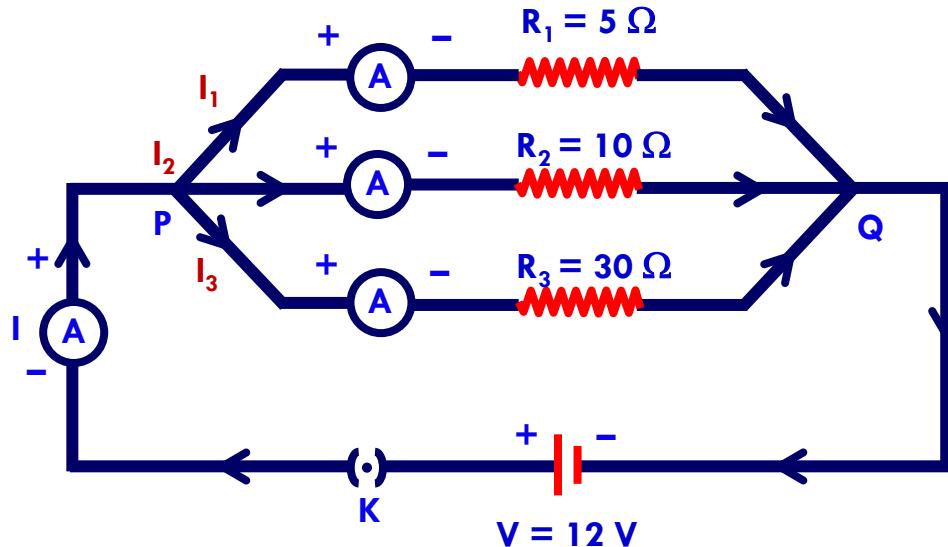In the circuit diagram given suppose the resistors R_1 , R_2 and R_3 have the values $5\ \Omega$, $10\ \Omega$ and $30\ \Omega$, respectively, which have been connected to a battery of 12 V . Calculate (a) the current through each resistor, (b) the total current, (c) the total resistance.



6

In the circuit diagram given suppose the resistors R_1 , R_2 and R_3 have the values $5\ \Omega$, $10\ \Omega$ and $30\ \Omega$, respectively, which have been connected to a battery of 12 V . Calculate (a) the current through each resistor, (b) the total current, (c) the total resistance.

Given :

$$R_1 = 5\ \Omega$$

$$R_2 = 10\ \Omega$$

$$R_3 = 30\ \Omega$$

$$V = 12\text{ V}$$

To find :


1. Effective resistance (R_p) = ?
2. Total current (I) = ?
3. Current in each resistor
i.e. I_1 , I_2 and I_3 .

Formulae :

$$1. \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$2. V = IR$$

Solution :

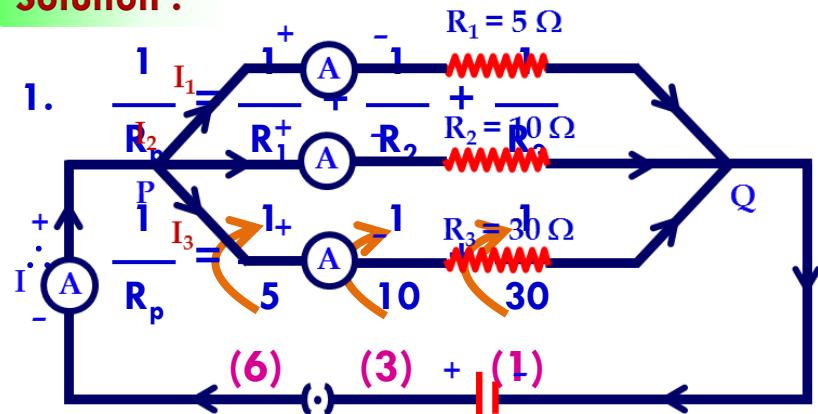

$$\therefore \frac{1}{R_p} = \frac{6 + 3 + 1}{30} \quad V = 12\text{ V}$$

$$\therefore \frac{1}{R_p} = \frac{10}{30}$$

$$\therefore R_p = \frac{30}{10}$$

$$\therefore R_p = 3\ \Omega$$

6

In the circuit diagram given suppose the resistors R_1 , R_2 and R_3 have the values $5\ \Omega$, $10\ \Omega$ and $30\ \Omega$, respectively, which have been connected to a battery of $12\ V$. Calculate (a) the current through each resistor, (b) the total current, (c) the total resistance.

$$2. \ I_1 = \frac{V}{R_1}$$

$$\therefore I_1 = \frac{12}{5}$$

$$\therefore I_1 = 2.4\ A$$

$$3. \ I_2 = \frac{V}{R_2}$$

$$\therefore I_2 = \frac{12}{10}$$

$$\therefore I_2 = 1.2\ A$$

Ans :

Effective resistance in parallel is $3\ \Omega$.

Total current is $4\ A$.

Current in each resistor is $2.4\ A$, $1.2\ A$, $0.4\ A$.

$$4. \ I_3 = \frac{V}{R_3}$$

$$\therefore I_3 = \frac{12}{30}$$

$$\therefore I_3 = 0.4\ A$$

$$5. \ I = I_1 + I_2 + I_3$$


$$\therefore I = 2.4 + 1.2 + 0.4$$

$$\therefore I = 4\ A$$

7

If in circuit diagram, $R_1 = 10\Omega$, $R_2 = 40\Omega$, $R_3 = 30\Omega$, $R_4 = 20\Omega$, $R_5 = 60\Omega$,
a 12 V battery is connected to the arrangement.

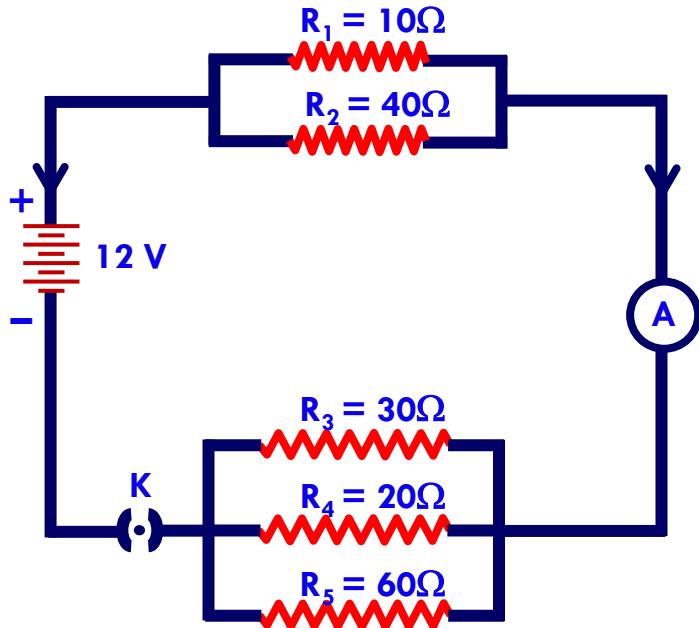Calculate (a) the total resistance (b) the total current flowing



7

If in circuit diagram, $R_1 = 10\Omega$, $R_2 = 40\Omega$, $R_3 = 30\Omega$, $R_4 = 20\Omega$, $R_5 = 60\Omega$, a 12 V battery is connected to the arrangement.

Calculate (a) the total resistance (b) the total current flowing

Given :

- $R_1 = 10\Omega$
- $R_2 = 40\Omega$
- $R_3 = 30\Omega$
- $R_4 = 20\Omega$
- $R_5 = 60\Omega$
- $V = 12V$

To find :

- Total resistance (R) = ?
- Total current (I) = ?

Formulae :

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I = \frac{V}{R}$$

Solution :


Let R_{P1} be the equivalent resistance of R_1 and R_2

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{P1}} = \frac{1}{10} + \frac{1}{40}$$

$$\therefore \frac{1}{R_{P1}} = \frac{4+1}{40} = \frac{5}{40}$$

$$\therefore R_{P1} = 8\Omega$$

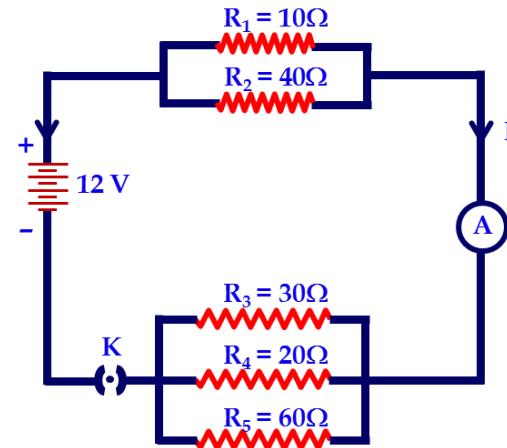

7

If in circuit diagram, $R_1 = 10\Omega$, $R_2 = 40\Omega$, $R_3 = 30\Omega$, $R_4 = 20\Omega$, $R_5 = 60\Omega$, a 12 V battery is connected to the arrangement.

Calculate (a) the total resistance (b) the total current flowing

Let R_{P2} be the equivalent resistance of R_3 , R_4 and R_5 then,

$$\frac{1}{R_{P2}} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

$$\therefore \frac{1}{R_{P2}} = \frac{1}{30} + \frac{1}{20} + \frac{1}{60}$$

$$\therefore \frac{1}{R_{P2}} = \frac{2+3+1}{60} = \frac{6}{60} = \frac{1}{10}$$

$$\therefore R_{P2} = 10\Omega$$

Ans :

The total resistance of the circuit is 18Ω and the total current is 0.67 A

Total resistance (R)

$$R = R_{P1} + R_{P2}$$

$$\therefore R = 8 + 10$$

$$R = 18\Omega$$


Total Current (I)

$$I = \frac{V}{R}$$

$$\therefore I = \frac{12}{18}$$

$$\therefore I = \frac{2}{3}$$

$$I = 0.67\text{ A}$$

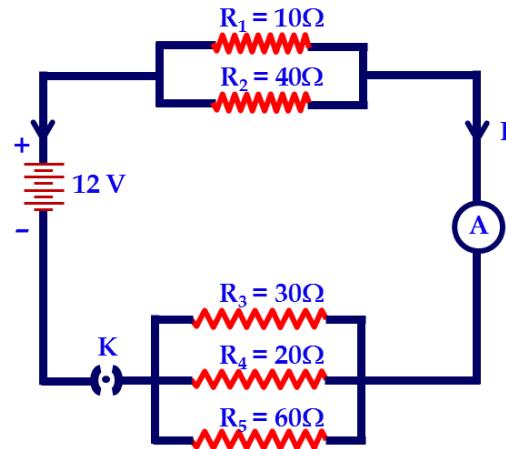

8

Show how you would connect three resistors, each of resistance $6\ \Omega$, so that the combination has a resistance of
 (i) $9\ \Omega$ (ii) $4\ \Omega$

Given : $R_1 = 6\ \Omega$

$$R_2 = 6\ \Omega$$

$$R_3 = 6\ \Omega$$

To find : How to connect to get:

$$(i) 9\ \Omega \quad (ii) 4\ \Omega$$

Formulae : $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$$R_s = R_1 + R_2 + R_3$$

Solution : (i) To get $9\ \Omega$:

(i) R_1 and R_2 are connected in parallel

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{6} + \frac{1}{6}$$

$$\frac{1}{R_p} = \frac{2}{6} \quad \therefore R_p = \frac{6}{2}$$

$$\therefore R_p = 3\ \Omega$$

Now R_p and R_3 are connected in series.

$$\therefore R = R_p + R_3$$

$$= 3 + 6 = 9\ \Omega$$

To get combination of $9\ \Omega$ R_1 and R_2 are connected in parallel and R_3 is connected in series with them

8

Show how you would connect three resistors, each of resistance $6\ \Omega$, so that the combination has a resistance of

- (i) $9\ \Omega$ (ii) $4\ \Omega$

Given : $R_1 = 6\ \Omega$

$R_2 = 6\ \Omega$

$R_3 = 6\ \Omega$

To find : How to connect to get:

- (i) $9\ \Omega$ (ii) $4\ \Omega$

Formulae : $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$$R_s = R_1 + R_2 + R_3$$

Solution : (ii) To get $4\ \Omega$:

(ii) R_1 and R_2 are connected in series.

$$R_s = R_1 + R_2$$

$$R_s = 6 + 6 = 12\ \Omega$$

Now R_s and R_3 are connected in parallel.

$$\begin{aligned}\frac{1}{R_p} &= \frac{1}{R_s} + \frac{1}{R_3} \\ &= \frac{1}{12} + \frac{1}{6} \\ &= \frac{1+2}{12}\end{aligned}$$

$$\frac{1}{R_p} = \frac{3}{12} \quad \therefore R_p = 4\ \Omega$$

To get combination of $4\ \Omega$ R_1 and R_2 are connected in series and R_3 is connected in parallel with them.

Q.9. What is (a) the highest, (b) the lowest total resistance that can be secured by combinations of four coils of resistance 4Ω , 8Ω , 12Ω , 24Ω ?

Given :

$$R_1 = 4\Omega$$

$$R_2 = 8\Omega$$

$$R_3 = 12\Omega$$

$$R_4 = 24\Omega$$

To find : (a) Highest equivalent resistance
(b) Lowest equivalent resistance

Solution : (a) To get highest equivalent resistance, these resistances should be connected in series.

$$\begin{aligned} R &= R_1 + R_2 + R_3 + R_4 \\ &= 4 + 8 + 12 + 24 \\ &= 48 \Omega \end{aligned}$$

(b) To get lowest equivalent resistance, these resistances should be connected in parallel.

$$\begin{aligned} \therefore \frac{1}{R} &= \frac{1}{4} + \frac{1}{8} + \frac{1}{12} + \frac{1}{24} \\ &= \frac{6+3+2+1}{24} \\ &= \frac{12}{24} = \frac{1}{2} \\ \therefore R &= 2 \Omega \end{aligned}$$

10

How many 176Ω resistors (in parallel) are required to carry 5 A on a 220 V line?

Given : Voltage (V) = 220 V

Current (I) = 5 A

Resistance of single resistor

To find : No. of resistors (n) = ?

Formulae : $V = IR$, $R_{eq} = \frac{R}{n}$

Formula for Equivalent
resistance of n resistors
connected in parallel

$$R_{eq} = \frac{R}{n}$$

$$n = \frac{R}{R_{eq}}$$

$$n = \frac{176}{44}$$

$$n = 4$$

Solution :

$$\begin{aligned}V &= IR \\R_{eq} &= \frac{V}{I} \quad \dots \dots (i) \\&= \frac{220}{5} \\&= 44 \Omega\end{aligned}$$

Ans :

4 resistors of 176Ω are required to draw the given amount of current.






Thank You

LECTURE 7

11

A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of $24\ \Omega$ resistances, which may be used separately, in series, or in parallel. What are the currents in the three cases ?

$$R=24\ \Omega$$

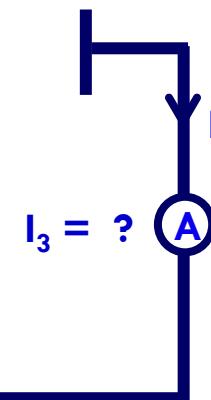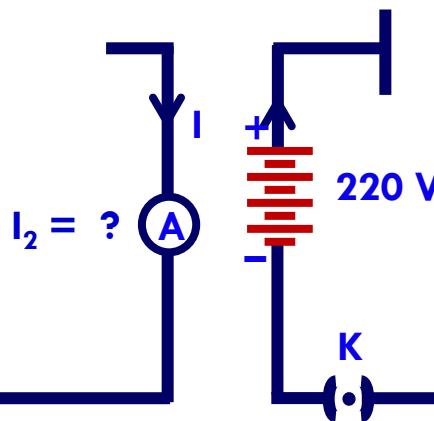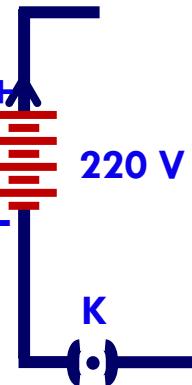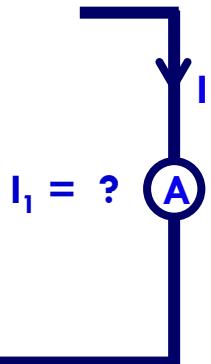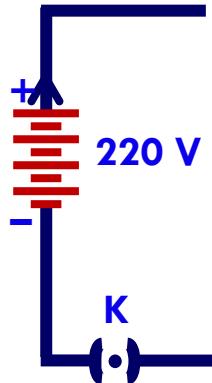

11

A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of $24\ \Omega$ resistances, which may be used separately, in series, or in parallel. What are the currents in the three cases ?

Given :

$$\text{Voltage (V)} = 220\ \text{V}$$

$$\text{Resistance (R)} = 24\ \Omega$$

To find :

$$\text{Current when coils are used separately (I}_1\text{)} = ?$$

$$\text{Current of series combination (I}_2\text{)} = ?$$

$$\text{Current of parallel combination (I}_3\text{)} = ?$$

Formulae :

$$V = IR$$

$$R_s = R_1 + R_2$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

Solution : **Case I :** Coils used separately

$$\therefore I_1 = \frac{V}{R} = \frac{220}{24}$$

$$\therefore I_1 = 9.166\ \text{A}$$

Case II : Coils in series

Total resistance in series

$$R_s = R + R$$

$$\therefore R_s = 24 + 24$$

$$\therefore R_s = 48\ \Omega$$

According to ohm's law

$$V = I_2 R_s$$

$$\therefore I_2 = \frac{V}{R_s} = \frac{220}{48}$$

Ans :

The currents flowing through the coils when they are used separately, in series and in parallel are 9.166 A, 4.58 A and 18.33 A respectively

Case III : Coils in parallel

Total resistance in parallel

$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R}$$

$$\therefore \frac{1}{R_p} = \frac{1}{24} + \frac{1}{24} = \frac{2}{24}$$

$$\therefore R_p = \frac{24}{2}$$

$$\therefore R_p = 12\ \Omega$$

According to ohm's law

$$V = I_3 R_p$$

$$\therefore I_3 = \frac{V}{R_p} = \frac{220}{12}$$

13 A



TYPE - B


$$V = IR$$

NUMERICAL


$$R = \frac{\rho l}{A} \quad (A = \pi r^2)$$

1

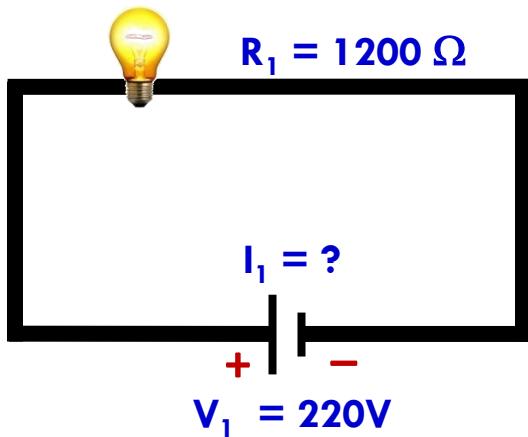- (a) How much current will an electric bulb draw from a 220 V source, if the resistance of the bulb filament is 1200Ω ?
- (b) How much current will an electric heater coil draw from a 220 V source, if the resistance of the heater coil is 100Ω ?



1st circuit

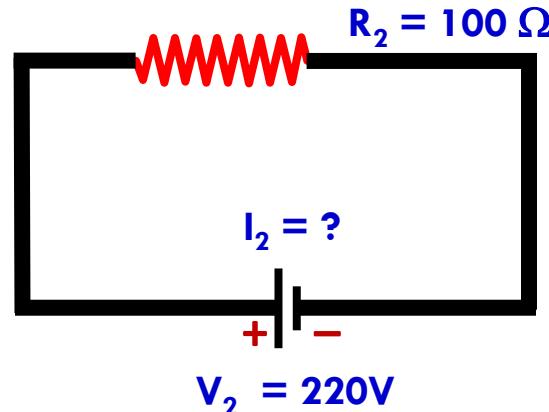

2nd circuit

1

- (a) How much current will an electric bulb draw from a 220 V source, if the resistance of the bulb filament is 1200 Ω ?
- (b) How much current will an electric heater coil draw from a 220 V source, if the resistance of the heater coil is 100 Ω ?

Given : $V_1 = 220 \text{ V}$; $R_1 = 1200 \Omega$, $V_2 = 220 \text{ V}$; $R_2 = 100 \Omega$.

To find : $I_1 = ?$ $I_2 = ?$

Formula: $V = IR$


Solution : $V_1 = I_1 R_1$

$$\therefore 220 = I_1 \times 1200$$

$$\therefore I_1 = \frac{220}{1200} = \frac{22}{120} = \frac{11}{60}$$

$$I_1 = 0.18 \text{ A}$$

Ans : Current through bulb is 0.18 A

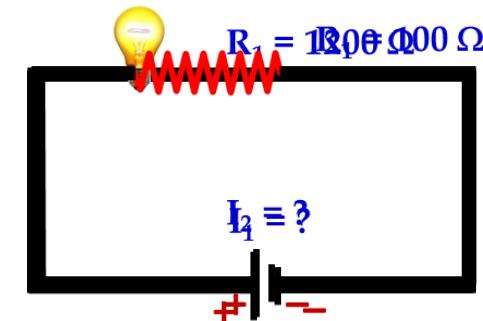

$$V_2 = I_2 R_2$$

$$\therefore 220 = I_2 \times 100$$

$$\therefore I_2 = \frac{220}{100} = \frac{22}{10}$$

2nd circuit

$$I_2 = 2.2 \text{ A}$$

Current through heater is 2.2 A

2

The potential difference between the terminals of an electric heater is 60 V when it draws a current of 4 A from the source. What current will the heater draw if the potential difference is increased to 120 V ?

Given : Potential difference (V) = 60 V

Current (I) = 4 A

Increased Potential difference (V_i) = 120 V

To find : Current (I) = ?

Formula : $V = IR$

Solution : $V = IR$

$$\therefore R = \frac{V}{I}$$

$$\therefore R = \frac{60}{4} \Omega$$

$$\therefore R = 15 \Omega$$

'V' is increased but
'R' remains constant

When V is increased to 120V then,

$$I = \frac{V_i}{R}$$
$$= \frac{120}{15} \Omega$$

$$\therefore I = 8 \text{ A}$$

Ans : The current in the heater is 8 A

3

Resistance of a metal wire of length 1 m is 26Ω at 20°C . If the diameter of the wire is 0.3 mm, what will be the resistivity of the metal at that temperature?

Ans :

$$(R) = 26 \Omega$$

$$(l) = 1\text{m}$$

$$(d) = 0.3 \text{ mm}$$

$$\therefore r = 0.15 \text{ mm}$$


$$= 15 \times 10^{-5}\text{m}$$

$$R = \rho \frac{l}{A}$$

$$\therefore \rho = \frac{R \times A}{l} = \frac{R \times \pi r^2}{l}$$

$$= \frac{26 \times 3.14 \times (15 \times 10^{-5})^2}{1}$$
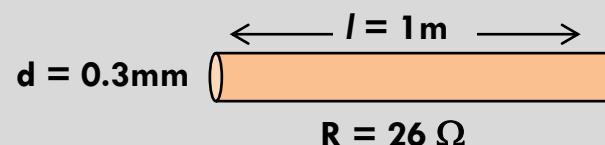
$$= 26 \times 3.14 \times 225 \times 10^{-6}$$



$$\rho = 1.84 \times 10^{-6} \Omega\text{m}$$

\therefore Resistivity of metal $= 1.84 \times 10^{-6} \Omega\text{m}$

4


A wire of given material having length l and area of cross section A has a resistance of 4Ω . What would be the resistance of another wire of the same material having length $l/2$ and area of cross section $2A$?

Ans : (i) For 1st wire :

$$R_1 = \rho \frac{l}{A} = 4 \Omega \dots \dots \dots \text{(i)}$$

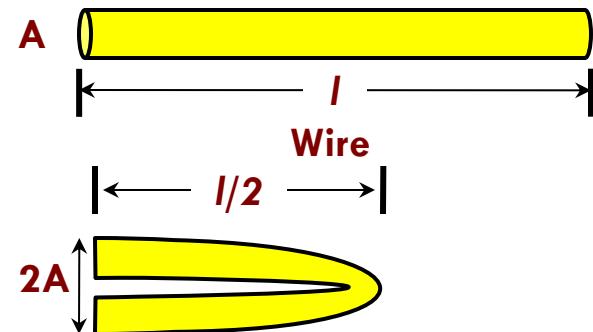(ii) For 2nd wire :

$$\begin{aligned} R_2 &= \rho \frac{l/2}{2A} \\ &= \frac{1}{4} \rho \frac{l}{A} \\ &= \frac{1}{4} \times R_1 \dots \dots \text{[from (i)]} \\ &= \frac{1}{4} \times 4 \end{aligned}$$



$\therefore R_2 = 1 \Omega \quad \therefore \text{The resistance of new wire is } 1 \Omega$

Q.5. When a 12V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

Given : $V = 12 \text{ V}$

$$I = 2.5 \text{ mA}$$

$$= 2.5 \times 10^{-3} \text{ A}$$

To find : $R = ?$

Formula : $R = \frac{V}{I}$

Solution : $R = \frac{12\text{V}}{2.5 \times 10^{-3}}$
 $= 4800 \Omega$

The value of the resistance of the resistor is 4800Ω

Q.6. Let the resistance of an electrical component remains constant while the potential difference across the two ends of the component decrease to half of its former value. What change will occur in the current through it?

Ans : According to Ohm's law,

$$V = IR$$

$$\therefore I = \frac{V}{R} \dots \dots \dots \text{(i)}$$

Now, the potential difference is reduced to half.

$$\text{New potential difference } V' = \frac{V}{2} \dots \dots \dots \text{(ii)}$$

∴ Resistance remains constant,

$$\text{New current } I' = \frac{V'}{R}$$

$$\text{New current } I' = \frac{V}{2R} \quad [\text{from(ii)}]$$

$$= \frac{1}{2} \times \frac{V}{R}$$
$$I' = \frac{1}{2} I$$

∴ The current through the component will also become half.


Q.7. (a) Draw a schematic diagram of a circuit consisting of a battery of three cells of 2 V each, a 5Ω resistor, an 8Ω resistor, and a 12Ω resistor and a plug key, all connected in series.

(b) Redraw the above circuit putting an ammeter to measure current through the resistors and a voltmeter to measure potential difference across 12Ω resistor. What would be the readings in ammeter and voltmeter.

Ans. : Since all the three resistors are in series,

(a) Total Resistance $R = 5 + 8 + 12\Omega$

$$= 25 \Omega$$

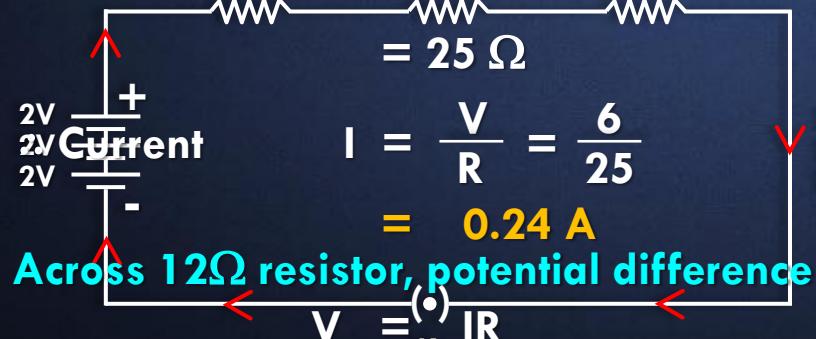

$$I = \frac{V}{R} = \frac{6}{25}$$

$$= 0.24 \text{ A}$$


Across 12Ω resistor, potential difference

$$V = IR$$

$$= 0.24 \times 12$$

$$= 2.88 \text{ V}$$

(b)

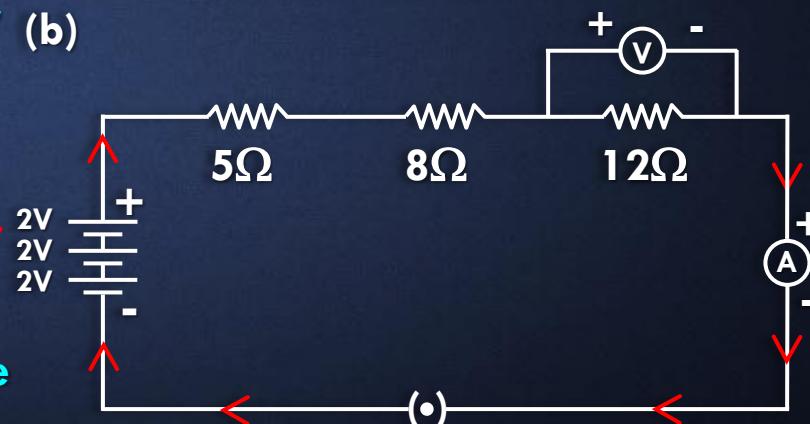

∴ Ammeter Reading = 0.24 A
Voltmeter Reading = 2.88 V

Thank You

LECTURE 8





Effects Of Electric Current

1st
Effect

Heating


2nd
Effect

Magnetic


3rd
Effect

Chemical

Heating Effect of Electric Current

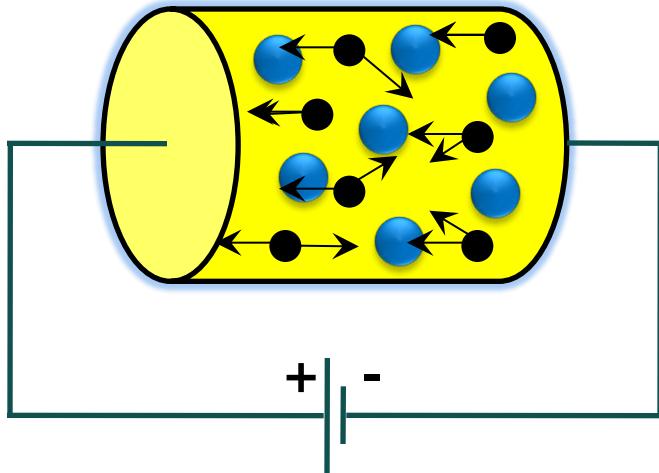

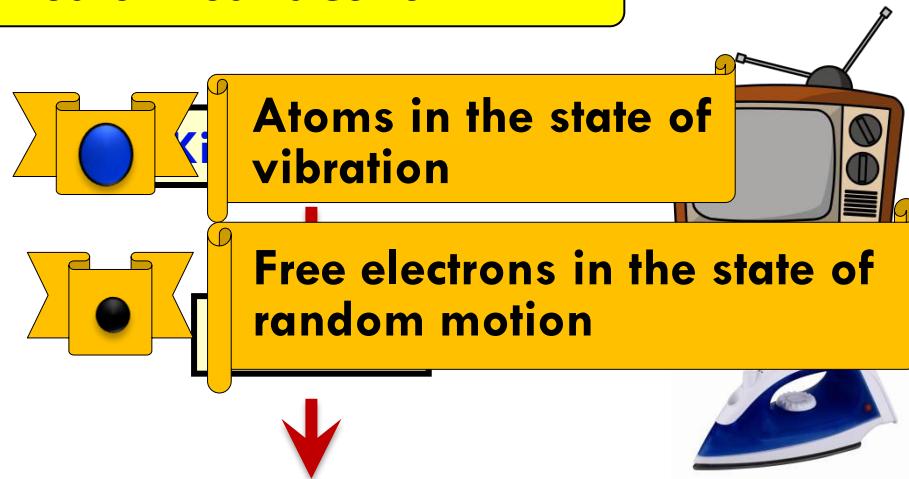But, according to law of conservation of energy, energy cannot be destroyed hence, this loss in kinetic energy is converted into heat energy



Heat energy



JOULE'S LAW

Heat produced in a resistor is directly proportional to


- Square of the current (I^2)
- Resistance of the conductor (R) and
- Time for which the current flows (t)

$$I = \frac{Q}{t}$$

$$\therefore Q = It \quad \dots \dots \dots (i)$$

$$\therefore V = IR \quad \dots \dots \dots (ii)$$
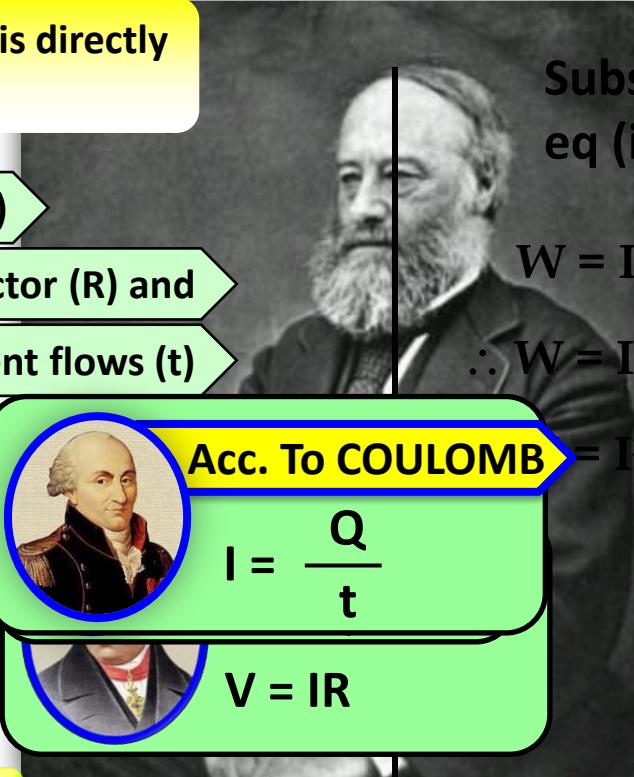
$$V = \frac{W}{Q} \quad \therefore W = VQ \quad \dots \dots \dots (iii) \text{ JOULE}$$



Substituting eq (i) and (ii) in eq (iii) we get

$$W = IR \cdot It$$

$$\therefore W = I^2 R t$$

oule

joule

W

Q

V

BRAIN TEASER

1. Which out of these is the right answer for Joule's law ?

(a)

$$H = VIt \text{ J}$$

(c)

$$H = I^2Rt \text{ J}$$

(b)

$$H = \frac{Vt}{R} \text{ J}$$

$$\therefore V = IR$$

$$\therefore H = IR \times It \text{ J}$$

$$\therefore H = I^2Rt \text{ J}$$


$$\frac{V^2t}{R} \text{ J}$$

$$\therefore H = \frac{I^2R^2 \times t}{R} \text{ J}$$

$$\therefore H = I^2Rt \text{ J}$$

APPLICATIONS OF HEATING EFFECT OF ELECTRIC CURRENT

ELECTRIC BULB

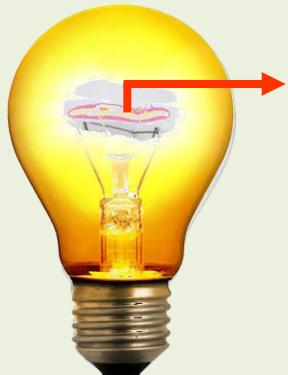

Filament made of tungsten

1

High Resistance

2

High Melting Point

3380°C

Chemically inactive nitrogen & argon




To Prevent oxidation



ELECTRIC IRON

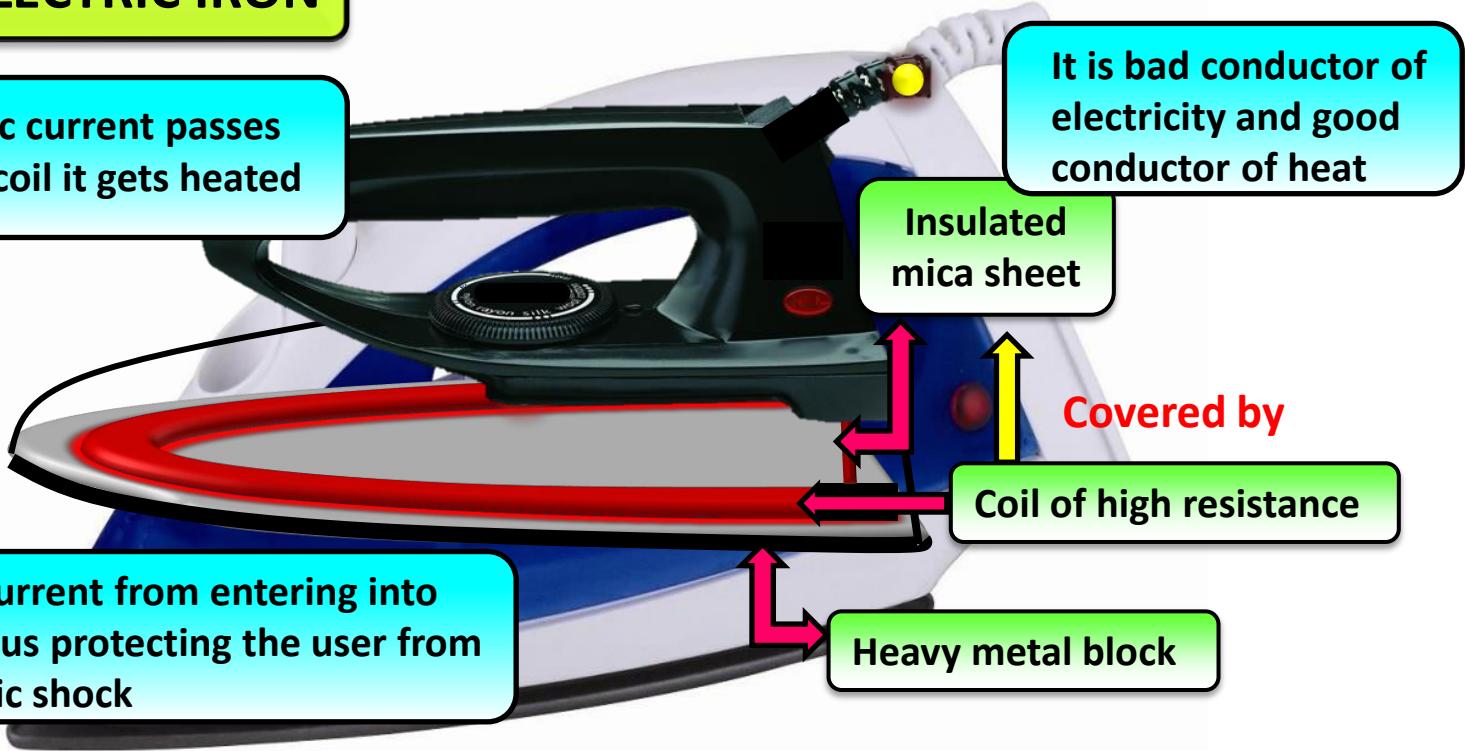When electric current passes through the coil it gets heated



It prevents the current from entering into the metal and thus protecting the user from getting an electric shock

It is bad conductor of electricity and good conductor of heat

Insulated
mica sheet

Covered by

Coil of high resistance

Heavy metal block

MAIN SUPPLY



ELECTRIC FUSE

The fuses used for domestic purposes are stated as 1A,2A,3A,4A,5A,10A etc.

An electric fuse protects circuits and appliances by stopping the flow of excess current.

Wire of Lead and Tin
(Low Melting Point)



Porcelain Body

Q.1. Why are coils of electric toasters and electric irons made of an alloy rather than a pure metal?

OR

Nichrome wire is used for making the heating elements of electrical appliances like iron, geyser, etc. Give reasons.

Ans. : Coils of electric toasters and irons are made of alloys rather than pure metals because :

- i. Resistivity of alloy is higher than pure metals.
- ii. Alloys have higher melting point, and so they don't melt easily.
- iii. Alloys do not oxidize at high temperature and thus can be kept red-hot.

Q.2. Why does the cord of an electric heater not glow while the heating element does?

- Ans. :**
- i. The heating element is made of alloy which has very high resistance. So when current flows through the element, it becomes very hot and glows.
 - ii. The cord is usually made of materials like copper and so has low resistance. Thus, for the same current, the cord does not become so hot and hence, does not glow.

Thank You

LECTURE 9



TYPE - D

Formulae based
on work done in joules

$$W = I^2Rt \text{ joule}$$

$$W = \frac{V^2t}{R} \text{ joule}$$

$$W = VIt \text{ joule}$$

$$\text{Power} = \frac{\text{Work done}}{\text{Time}}$$

$$P = \frac{I^2Rt}{t} \text{ watt}$$

$$P = \frac{V^2}{R} \text{ watt}$$

$$P = VI \text{ watt}$$

1

100 J of heat is produced each second in a 4Ω resistance. Find the potential difference across the resistor.

Given : Heat (H) = 100 J

Resistance (R) = 4Ω

Time (t) = 1 sec

To find : P.D. (V) = ?

Formula : $H = \frac{V^2t}{R}$ J

Solution : $H = \frac{V^2t}{R}$ J

$$\therefore V = \sqrt{\frac{H \times R}{t}}$$

$$\therefore V = \sqrt{\frac{100 \times 4}{1}}$$

$$\therefore V = \sqrt{400}$$

$$H = I^2Rt \text{ J}$$

$$H = \frac{V^2t}{R} \text{ J}$$

$$H = VIt \text{ J}$$

$$\therefore V = 20 \text{ V}$$

Ans : Potential difference across the resistor is 20 V.

2

Compute the heat generated while transferring 96000 coulomb of charge in one hour through a potential difference of 50 V.

Given : P.D. (V) = 50 V

$$\text{Time (t)} = 1 \text{ hr} = 1 \times 60 \times 60 \text{ s}$$

$$\text{Charge (Q)} = 96000 \text{ C}$$

To find : Heat (H) = ?

$$\text{Formulae : } I = \frac{Q}{t}$$

$$H = VIt$$

$$\text{Solution : } I = \frac{Q}{t}$$

$$\therefore I = \frac{\cancel{80}}{\cancel{160}} \frac{\cancel{96000}}{\cancel{60 \times 60}} \frac{1}{3}$$

$$\therefore I = \frac{80}{3} \text{ A}$$

$$H = VIt$$

$$\therefore H = 50 \times \frac{80}{3} \times \cancel{60} \times 60$$

$$\therefore H = 4800000$$

$$\therefore H = 4.8 \times 10^6 \text{ J}$$

$$H = I^2Rt \text{ joule}$$

$$H = \frac{V^2t}{R} \text{ joule}$$

$$H = VIt \text{ joule}$$

Ans : Heat generated is $4.8 \times 10^6 \text{ J}$

3

An electric iron of resistance 20Ω takes a current of 5 A . Calculate the potential difference and heat developed in 30 s .

Given : Current (I) = 5 A

Time (t) = 30 s

Resistance (R) = 20Ω

To find : Heat (H) = ?

P.D (V) = ?

Formulae : $V = IR$

$H = VIt$

Solution : $V = IR$

$$\therefore V = 5 \times 20$$

$$\therefore V = 100 \text{ V}$$

$$H = I^2Rt \text{ joule}$$

$$H = \frac{V^2t}{R} \text{ joule}$$

$$H = VIt$$

$$\therefore H = 100 \times 5$$

$$\therefore H = 15000$$


$$\therefore H = 1.5 \times 10^4 \text{ J}$$

Ans :

The amount of heat developed in the electric iron is $1.5 \times 10^4 \text{ J}$

4

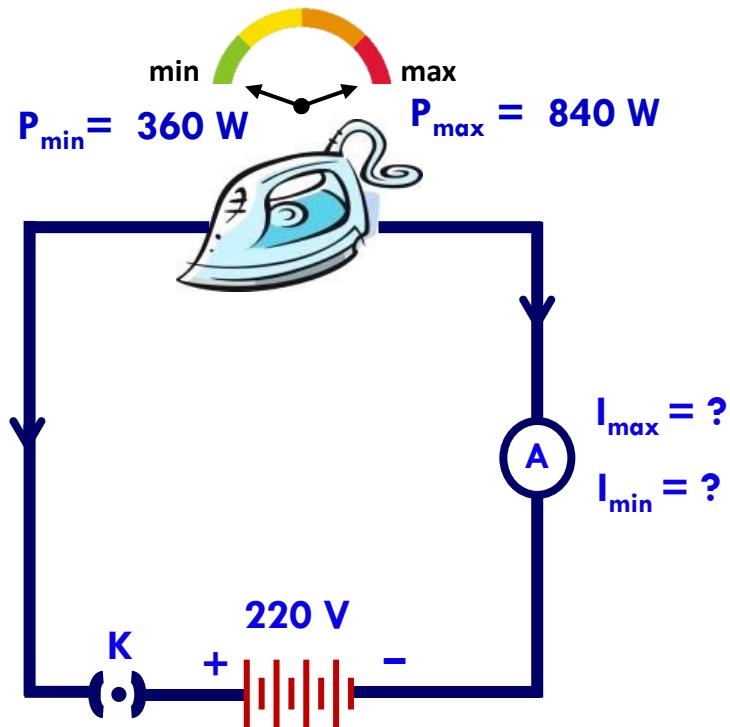An electric iron consumes energy at a rate of 840 W when heating is at the maximum rate and 360 W when the heating is at the minimum. The voltage is 220 V. What is the current in each case?



4

An electric iron consumes energy at a rate of 840 W when heating is at the maximum rate and 360 W when the heating is at the minimum. The voltage is 220 V. What is the current in each case?

Given : Power at maximum rate (P_{\max}) = 840 W

Power at minimum rate (P_{\min}) = 360 W

Potential Difference (V) = 220 V

To find : I_{\max} = ?

I_{\min} = ?

Formula : $P = VI$

Solution : When heating is at the maximum rate: $P_{\max} = 840$ W, $V = 220$ V

$$P_{\max} = VI_{\max}$$

$$\therefore I_{\max} = \frac{P_{\max}}{V}$$

$$\therefore P = I^2R \text{ watt}$$

$$\therefore P = \frac{V^2}{R} \text{ watt}$$

When heating is at the minimum rate:

$$P_{\min} = VI \text{ watt}$$


$$\therefore I_{\min} = \frac{P_{\min}}{V}$$

$$\therefore I_{\min} = 1.64 \text{ A}$$

Ans : $I_{\max} = 3.82 \text{ A}$,
 $I_{\min} = 1.64 \text{ A}$.

5

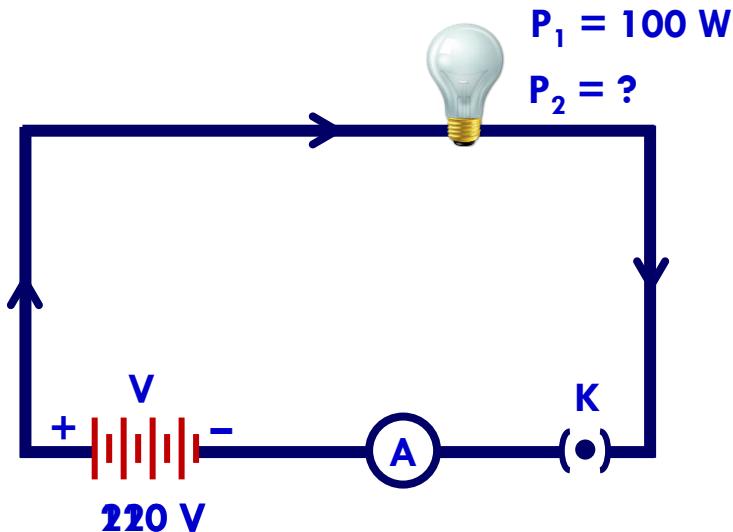An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be ?



5

An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be ?

Given : Power (P_1) = 100 W

P.D. (V_1) = 220 V

P.D. (V_2) = 110 V

To find : Power (P_2) = ?

Formula : $P = \frac{V^2}{R}$

Solution : $P_1 = \frac{V_1^2}{R}$

$$\therefore 100 = \frac{(220)^2}{R}$$

$$\therefore R = \frac{220 \times 220}{100}$$

$$\therefore R = 484 \Omega$$

Resistance remains constant even at 110 V

$$\therefore P_2 = \frac{V_2^2}{R}$$

$$\therefore P_2 = \frac{(110)^2}{484}$$

$$\therefore P_2 = \frac{\cancel{110} \times \cancel{110}}{\cancel{484}}$$


~~5~~
~~55~~
~~242~~
~~121~~
~~11~~
1

$$\therefore P_2 = 25 \text{ W}$$

Ans : The power consumed at 110 V is 25 W.

6

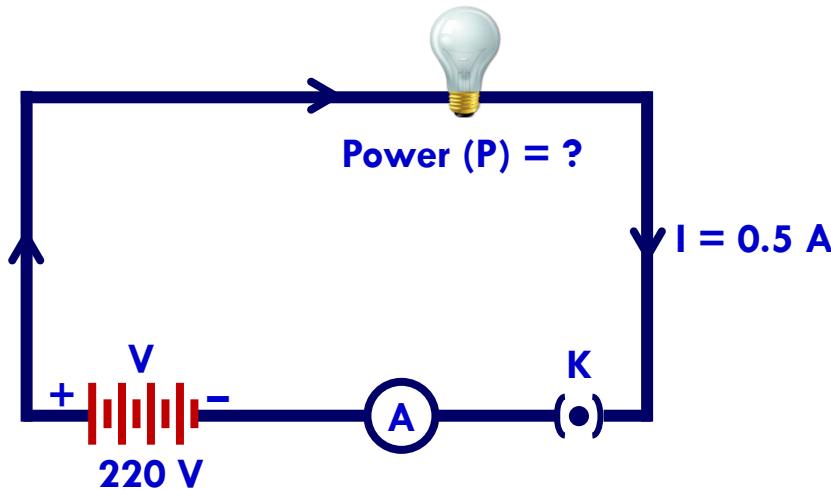An electric bulb is connected to a 220 V generator. The current is 0.50 A. What is the power of the bulb?



6

An electric bulb is connected to a 220 V generator. The current is 0.50 A. What is the power of the bulb?

Given : Current (I) = 0.50 A

P.D. (V) = 220 V

To find : Power (P) = ?

Formula : $P = VI$

Solution : $P = VI$

$$\therefore P = 220 \times 0.50$$

$$\therefore P = 110 \text{ W}$$

$$P = I^2R \text{ watt}$$

$$P = VI \text{ watt}$$

$$P = \frac{V^2}{R} \text{ watt}$$

Ans : Power of the bulb is 110 W.

7

An electric heater of resistance 8Ω draws $15 A$ from the service mains for 2 hours. Calculate the rate at which heat is developed in the heater.

Given : Resistance (R) = 8Ω

Current (I) = $15 A$

To find : Power (P) = ?

Formula : $P = I^2R$

Solution : $P = I^2R$


$$\therefore P = (15)^2 \times 8$$

$$\therefore P = 1800 \text{ J/s}$$

Ans : Heat is produced by the heater at the rate of 1800 J/s

8

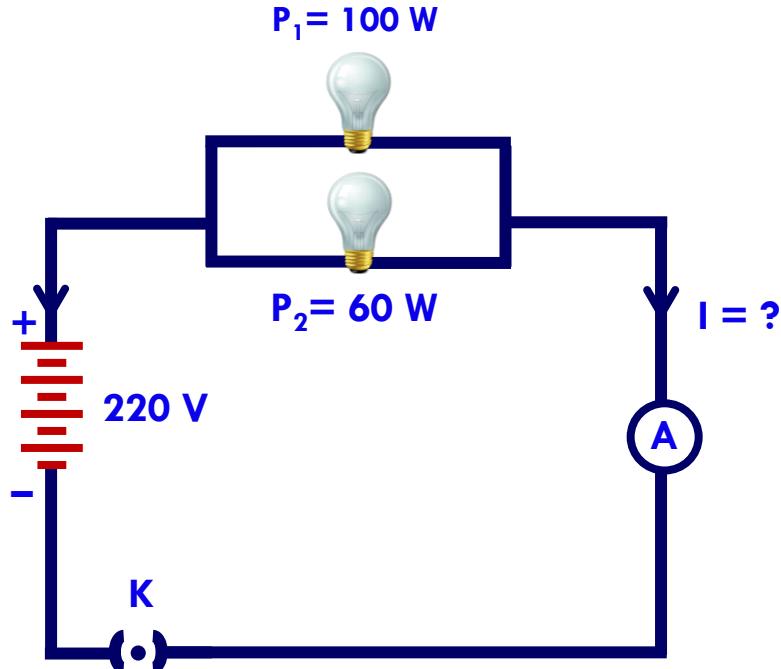Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V ?



8

Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V ?

Given : Power (P_1) = 100 W

Power (P_2) = 60 W

P. D. (V) = 220 V

To find : Current (I) = ?

Formula : $P = VI$

Solution : Current drawn by the bulb of rating 100 W is

$$P_1 = VI_1$$

$$\therefore I_1 = \frac{P_1}{V}$$

$$\therefore I_1 = \frac{100}{220} A$$

Similarly, Current drawn by the bulb of rating 60 W is

$$P_2 = VI_2$$

$$\therefore I_2 = \frac{P_2}{V}$$

$$\therefore I_2 = \frac{60}{220} A$$

$$\begin{aligned}\text{Current drawn from the line} &= I_1 + I_2 \\ &= \frac{100}{220} + \frac{60}{220} \\ &= 0.727 A\end{aligned}$$

Ans : Current drawn from the line is 0.727 A

Q.5. Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel combination would be : (a) 1:2 (b) 2:1 (c) 1:4 (d) 4:1

Ans. : (c) 1:4

Let R_s be the equivalent resistances of the wire when connected in series and R_p be the equivalent resistance, when connected in parallel.

$$\therefore R_s = R + R = 2R$$

$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} = \frac{2}{R}$$

$$\frac{1}{R_p} = \frac{R}{2}$$

$$H = \frac{V^2 t}{R}$$

$$\begin{aligned}\therefore \frac{H_s}{H_p} &= \frac{\frac{V^2 t}{R_s}}{\frac{V^2 t}{R_p}} \\ &= \frac{R_p}{R_s} \\ \therefore \frac{H_s}{H_p} &= \frac{1}{4}\end{aligned}$$

Thank You

LECTURE 10

Electric power is the rate at which electric energy is dissipated or consumed in an electric circuit

❖ Relation between Commercial & S.I. unit of work

$$1\text{ kW h} = 1000 \text{ W} \times 3600 \text{ s}$$

$$1\text{ kW h} = 36 \times 10^5 \text{ W - S}$$

$$1\text{ kW h} = 36 \times 10^5 \text{ joule}$$

$$1\text{ kW h} = 3.6 \times 10^6 \text{ J}$$

Power

$\frac{\text{work}}{\text{time}}$

Electric power

Energy consumed

time

What is kWh

Energy consumed

Unit of electric energy

watt × second

Energy consumed in bigger units

1 kW × 1 h

1 Unit



TYPE - E

$$\text{Electric Power} = \frac{\text{Energy Consumed}}{\text{time in hours}}$$

Note : Electric power should be in kilowatts & time should be in hours

1

An electric refrigerator rated 400 W operates 8 hour/day. What is the cost of the energy to operate it for 30 days at Rs 3.00 per kWh?

Given : Power (P) = 400 W = $\frac{400}{1000}$ kW = 0.4 kW Ans :

Time (t) = $30 \times 8\text{ h} = 240\text{ h}$

Cost per kWh = Rs 3

The cost of energy to operate the refrigerator for 30 days is Rs. 288

To find : Energy consumed = ?

Formulae : Energy consumed = P × t

Solution : Energy consumed = P × t

Energy consumed = 0.4 kW × 240 h

Energy consumed = 96 kWh

Cost of energy = 96 × 3

Cost of energy = Rs. 288

2

An electric heater rated 1000W / 220V operates 2 hours daily. Calculate the cost of energy to operate for 30 days at Rs. 3 per kWh.

Given : Power (P) = 1000W = 1 kW

Time (t) = 2 h/day

To find : Cost of energy to operate for 30 days = ?

Formula : Energy consumed = $P \times t$

Solution : Energy consumed by electric heater

$$\begin{aligned} &= P \times t \\ &= 1 \text{ kW} \times 2 \text{ h} \\ &= 2 \text{ kWh} \end{aligned}$$

Cost of energy to operate = $2 \times 3 = \text{Rs. 6 per day}$

Cost of energy to operate for 30 days = $30 \times 6 = \text{Rs. 180}$

Ans : Cost of energy to operate electric heater for 30 days is Rs. 180

3

A 100 watt electric bulb is lighted for 2 hours daily and four 40 watt bulbs are lighted for 4 hours everyday. Calculate the energy consumed.

Given : Power (P_1) = 100 Watt = $\frac{100}{1000}$ kW
time (t_1) = 2 hours
Power (P_2) = 40 Watt = $\frac{40}{1000}$ kW
time (t_2) = 4 hours

To find : Energy consumed in each case?

Formula : Energy consumed = Power × time

Solution : Energy consumed = $P_1 \times t_1$
= $0.1 \text{ kW} \times 2 \text{ h}$
= 0.2kWh

Energy consumed by 100 watt bulb in one day is 0.2kWh

$$\begin{aligned}\text{Energy consumed} &= 4 \times P_2 \times t_2 \\&= 4 \times 0.04 \text{ kW} \times 4 \text{ h} \\&= 0.64 \text{ kWh}\end{aligned}$$

Energy consumed by four 40 watt bulbs in one day is 0.64kWh

$$\begin{aligned}\text{Total Energy consumed} &= 0.2 + 0.64 \\&= 0.84 \text{kWh}\end{aligned}$$

Ans : Total Energy consumed is 0.84kWh

4

Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes ?

Given : Power (P_1) = 250 W = $\frac{250}{1000}$ kW

Power (P_2) = 1200 W = $\frac{1200}{1000}$ kW

Time (t_1) = 1 h

Time (t_2) = 10 min = $\frac{10}{60}$ h
= 0.167 h

To find : Energy consumed = ?

Formula : Energy consumed = Pt

Solution : Energy consumed by a 250 W TV set in 1 h = $P_1 \times t_1$
= $0.25 \text{ kW} \times 1 \text{ h}$
= 0.25 kWh

Energy consumed by 1200 W toaster in 10 min = $P_2 \times t_2$
= $1.2 \text{ kW} \times 0.167 \text{ h}$
= 0.2 kWh

Ans :

Energy consumed by a 250 W TV set in 1 hr is more than the energy consumed by a 1200 W toaster in 10 minutes

5

A household uses the following electric appliances :

- (i) Refrigerator of rating 400W for ten hours each day
- (ii) Two electric fans of rating 80W for 12 hours each day
- (iii) Six electric tubes of rating 18 W each for 6 hours each days

Calculate the electricity bill of the household for the month of June.

If the cost per unit of electric energy is Rs. 5.00 per kwh

Given : Power (P_1) = 0.4 kW; $t_1 = 10$ h/day

Power (P_2) = 0.08 kW; $t_2 = 12$ h/day

Power (P_3) = 0.018 kW; $t_3 = 6$ h/day

Cost per unit of
electric energy = Rs. 5.00

To find : Electricity bill of household = ?

Formula : Energy consumed = $P \times t$

Solution : Energy consumed by refrigerator = $P_1 \times t_1$
 $= 0.4 \times 10$
 $= 4$ kWh

Energy consumed by two electric fans = $2 \times P_2 \times t_2$
 $= 2 \times 0.08 \times 12 = 1.92$ kWh

Energy consumed by six electric tubes = $6 \times P_3 \times t_3$
 $= 6 \times 0.018 \times 6 = 0.648$ kWh

Total electrical energy consumed = $4 + 1.92 + 0.648$
 $= 6.568$ kWh

Total electrical energy consumed in month of June (30 days) = $6.568 \text{ kWh} \times 30$

Ans :

Electricity bill of household for month of June is Rs. 985.20

Thank You

LECTURE 11

1

Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A?

Given : P.D. (V) = 220 V

Maximum current, (I_{\max}) = 5 A

Power of one bulb (P_1) = 10 W

To find : No. of bulbs to be connected in parallel (x)

Formulae : $P = \frac{V^2}{R}$, $V = IR$, $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_x}$

Solution : Resistance R_1 , of the bulb is given by the expression,

$$P_1 = \frac{V^2}{R_1} \quad R_1 = \frac{V^2}{P_1}$$

$$R_1 = \frac{(220)^2}{10} = 4840 \Omega \quad \dots \text{(i)}$$

According to Ohm's law,

$$V = IR$$

R is the total resistance of the circuit for x number of electric bulbs

$$R = \frac{V}{I} = \frac{220}{5} = 44 \Omega \quad \dots \text{(ii)}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_x}$$

From eq. (i) and (ii),

$$x = \frac{R_1}{R} = \frac{4840}{44} = 110$$

Ans : 110 electric bulbs are connected in parallel.

2

A copper wire has a diameter of 0.5 mm and resistivity of $1.6 \times 10^{-8} \Omega \text{ m}$.

(a) What will be the length of this wire to make its resistance 10Ω ?

(b) How much does the resistance change if the diameter is doubled?

$$(b) R \propto \frac{1}{d^2}$$

So, when the diameter of the wire is doubled, then its resistance will become $(1/2)^2$ or $1/4$

To find : (a) Length (l) = ?

(b) How much does the resistance change if the diameter is doubled?

Formula : $R = \frac{\rho l}{A}$, $A = \pi r^2$

Solution : $R = \frac{\rho l}{A}$

$$\rho = \frac{R \times A}{l} \quad \therefore l = \frac{R \times \pi r^2}{\rho} = \frac{1.6 \times 10^{-8} \Omega \text{ m}}{\rho}$$

$$l = \frac{10 \times 3.14 \times (0.25 \times 10^{-3})^2}{1.6 \times 10^{-8}}$$

$$= \frac{10 \times 3.14 \times 0.0625 \times 10^{-6}}{0.8 \times 1.6 \times 10^{-8}}$$


$$= \frac{10 \times 1.57 \times 0.0625 \times 10^{-6} \times 10^8}{0.8}$$

$$= \frac{10 \times 1.57 \times 0.0625 \times 10^2}{0.8}$$

$$l = \frac{1.57 \times 62.5}{0.8} \quad \therefore l = 122.65 \text{ m}$$

3

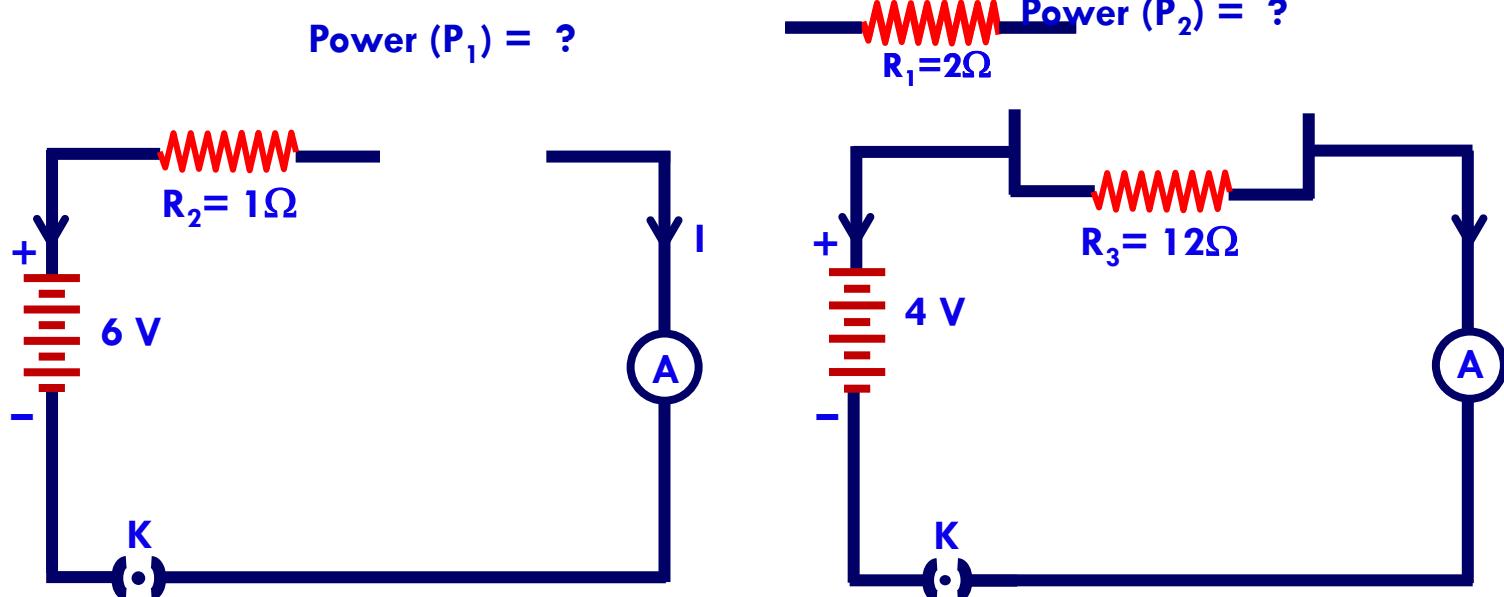Compare the power used in the 2Ω resistor in each of the following circuits : (i) a 6 V battery in series with 1Ω and 2Ω resistors, and (ii) a 4 V battery in parallel with 12Ω and 2Ω resistors.



Current in both the circuit is I , resistance is 2Ω hence by using the formula $P=I^2R$, Power used in both cases will be the same.

3

Compare the power used in the $2\ \Omega$ resistor in each of the following circuits : (i) a 6 V battery in series with $1\ \Omega$ and $2\ \Omega$ resistors, and (ii) a 4 V battery in parallel with $12\ \Omega$ and $2\ \Omega$ resistors.

Given :

- Resistance (R_1) = $2\ \Omega$
- Resistance (R_2) = $1\ \Omega$
- Resistance (R_3) = $12\ \Omega$
- P.D. (V_1) = 6 V
- P.D. (V_2) = 4 V

To find :

- Power (P_1) = ?
- Power (P_2) = ?

Formulae :

- $R_s = R_1 + R_2$
- $V_1 = IR_s$
- $P_1 = I^2R_1$

Ans : The power used by $2\ \Omega$ resistor in both the cases is 8 watt

Solution :

Case I : $1\ \Omega$ and $2\ \Omega$ resistors are connected in series

$$R_s = R_1 + R_2$$

$$\therefore R_s = 1 + 2$$

$$\therefore R_s = 3\ \Omega$$

$$V_1 = IR_s$$

$$\therefore 6 = I \times 3$$

$$\therefore I = 2\ A$$

$$P_1 = I^2R_1$$

$$P_1 = (2)^2 \times 2$$

$$P_1 = 8\ \text{watt}$$

Case II : $12\ \Omega$ and $2\ \Omega$ resistors are connected in parallel

In parallel combination potential difference remains same.

\therefore potential difference across $2\ \Omega$ resistor will be 2 V

$$P_2 = \frac{V_2^2}{R_1}$$

$$\therefore P_2 = \frac{(4)^2}{2}$$

$$\therefore P_2 = 8\ \text{watt}$$

Q.4. Calculate the effective resistance between P and Q.


Ans. : $R_{PAQ} = 7 + 3 = 10 \Omega$

$R_{PBQ} = 6 + 4 = 10 \Omega$

Now, 10Ω , 1Ω and 10Ω resistances are in parallel between P and Q.

$$\begin{aligned}\therefore \frac{1}{R} &= \frac{1}{10} + \frac{1}{1} + \frac{1}{10} \\ &= \frac{1 + 10 + 1}{10} = \frac{12}{10}\end{aligned}$$

or $R = \frac{5}{6} \Omega$

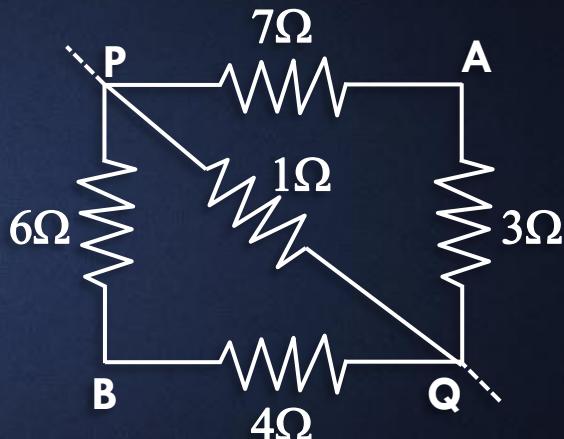

Q.5 Five resistors are connected as shown in the figure.
Find the ammeter reading when the circuit is closed.

Ans. : i. Between B and D

$$R_s = 3 + 3 = 6 \Omega$$

$$\frac{1}{R_p} = \frac{1}{R_s} + \frac{1}{3} = \frac{1}{6} + \frac{1}{3} = \frac{3}{6} = \frac{1}{2}$$


$$R_p = 2 \Omega$$

ii. Between A and E

$$R_s = 0.5 + 2 + 0.5 = 3 \Omega$$

$$\therefore I = \frac{V}{R} = \frac{3}{3}$$

Ammeter reading = 1 A

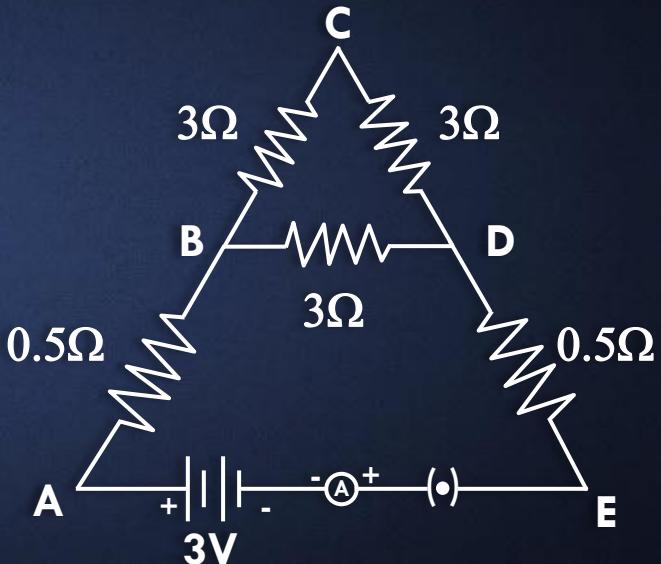

Thank You